

Pre Lab Worksheet (Exp 1)

Question 1: Kindly apply the KVL or KCL to find the value of all the branch current (I_1 to I_5), if the DC power supply1 voltage is the last two digits of your roll number. (Example: for the Roll number: REX124A15 Supply1 is 15 V)

