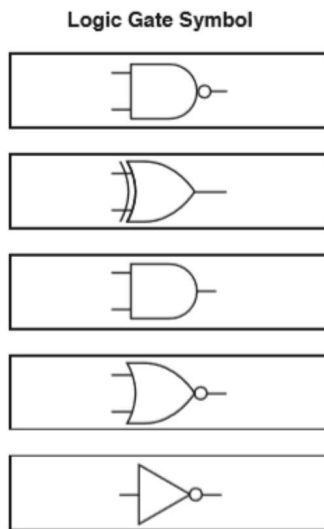


## Pre Lab Worksheet (Exp 9)

### Question 1:

- a) Write the name of the logic gates corresponding to each symbol



- b) Complete the truth table for the given circuit and write a logical statement

