
CSE211

**Computer Organization and
Design**

Lecture : 3

Tutorial: 1

Practical: 0

Credit: 4

Unit 1 : Basics of Digital Electronics

- Decoder
- Encoder
- Multiplexers
- Demultiplexer
- Binary Counter
- Registers

2-2 Decoder/Encoder

■ Decoder


- ◆ A combinational circuit that converts binary information from the n coded inputs to a maximum of 2^n unique outputs
- ◆ n -to- m line decoder = $n \times m$ decoder
 - n inputs, m outputs
- ◆ If the n -bit coded information has unused bit combinations, the decoder may have less than 2^n outputs
 - $m \leq 2^n$

■ 3-to-8 Decoder

- ◆ A Binary-to-octal conversion
- ◆ Logic Diagram : *Fig. 2-1*
- ◆ Truth Table : *Tab. 2-1*
- ◆ Commercial decoders include one or more Enable Input(E)

Enable	Inputs			Outputs							
E	A2	A1	A0	D7	D6	D5	D4	D3	D2	D1	D0
0	x	x	x	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0

Tab. 2-1 Truth table for 3-to-8 Decoder

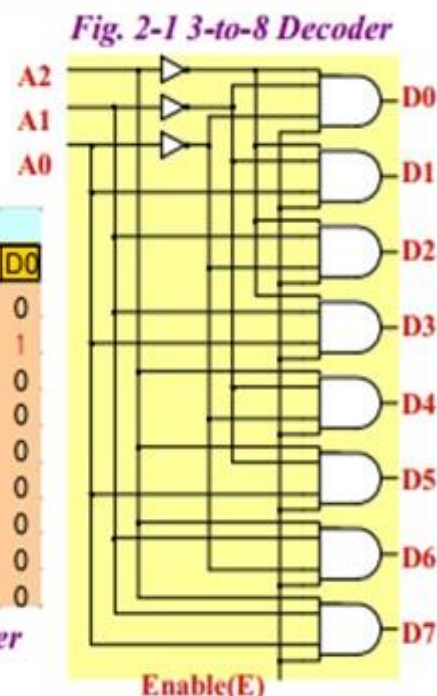

2-2 Decoder/Encoder

■ NAND Gate Decoder


- Active Low Output
- Fig. 2-1 3-to-8 Decoder \equiv Active High Output

- ◆ Constructed with NAND instead of AND gates
- ◆ Logic Diagram/Truth Table : *Fig. 2-2*

Fig. 2-2 2-to-4 Decoder with NAND gates

Enable Input		Output			
E	A1 A0	D0	D1	D2	D3
0	0 0	0	1	1	1
0	0 1	1	0	1	1
0	1 0	1	1	0	1
0	1 1	1	1	1	0
1	x x	1	1	1	1

(a) Truth Table

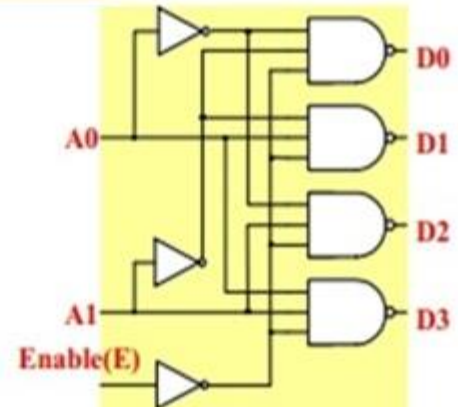

(b) Logic Diagram

■ Decoder Expansion

- ◆ Constructed decoder : *Fig. 2-3*
- ◆ 3 X 8 Decoder constructed with two 2 X 4 Decoder

■ Encoder

- ◆ Inverse Operation of a decoder
- ◆ 2^n input, n output
- ◆ Truth Table : *Tab. 2-2*

● 3 OR Gates Implementation

- » $A0 = D1 + D3 + D5 + D7$
- » $A1 = D2 + D3 + D6 + D7$
- » $A2 = D4 + D5 + D6 + D7$

Tab. 2-2 Truth Table for Encoder

Inputs								Outputs		
D7	D6	D5	D4	D3	D2	D1	D0	A2	A1	A0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

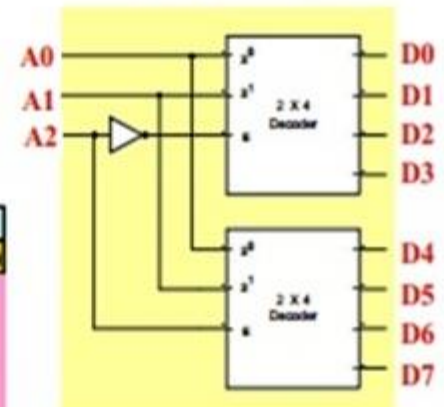


Fig. 2-3 A 3-to-8 Decoder constructed with two 2-to-4 Decoder

2-2 Decoder/Encoder


Octal to Binary Encoder

D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	A ₂	A ₁	A ₀
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1

$$A_0 = D_1 + D_3 + D_5 + D_7$$

$$A_1 = D_2 + D_3 + D_6 + D_7$$

$$A_2 = D_4 + D_5 + D_6 + D_7$$

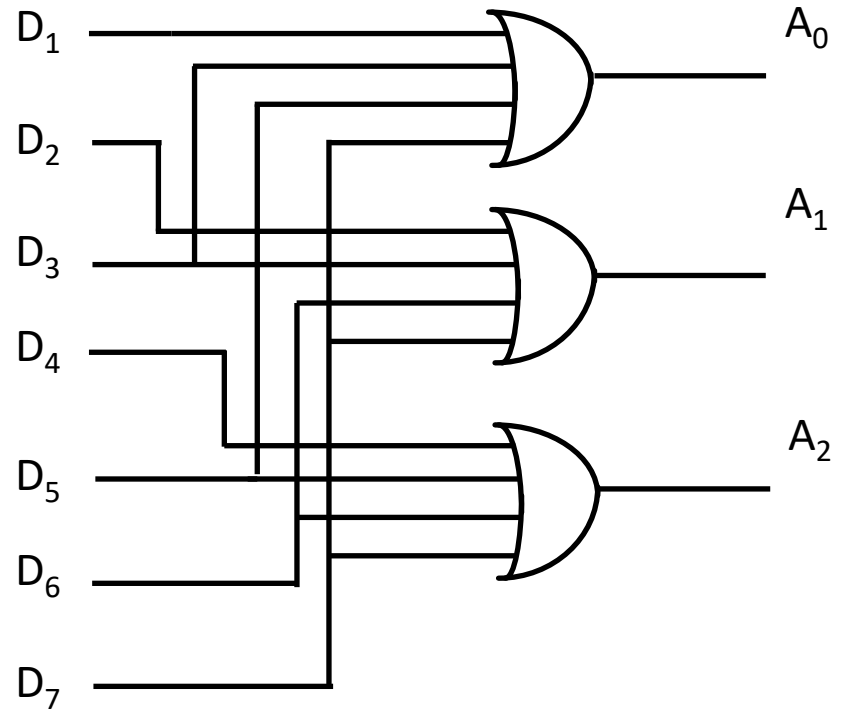

HALF ADDER

- Performs arithmetic addition of two bits.
- Input variables are called as AUGEND and ADDEND
- Output Variables are SUM and CARRY

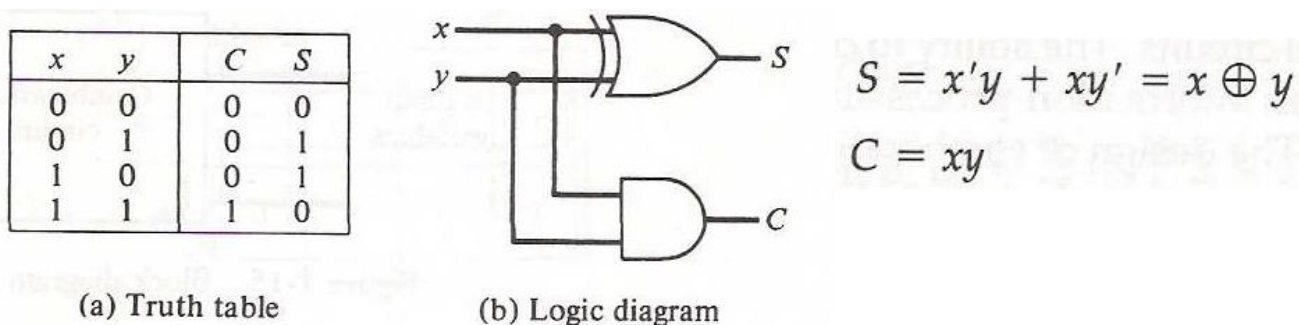


Figure 1-16 Half-adder.

FULL ADDER

- Performs arithmetic addition of three bits.
- Consists of three inputs and two outputs.

TABLE 1-2 Truth Table for Full-Adder

Inputs			Outputs	
<i>x</i>	<i>y</i>	<i>z</i>	<i>C</i>	<i>S</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


FULL ADDER

$$S = x \oplus y \oplus z$$

$$C = xy + (x \oplus y)z$$

• or

$$C = xy + (x'y + xy')z$$

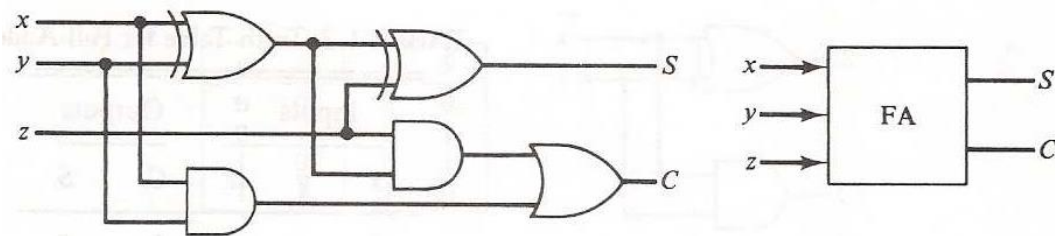

(a) Logic diagram

(b) Block diagram

Figure 1-18 Full-adder circuit.

2-3 Multiplexers

■ Multiplexer(Mux)

- ◆ A combinational circuit that receives binary information from one of 2^n input data lines and directs it to a single output line
- ◆ A 2^n -to 1 multiplexer has 2^n input data lines and n input selection lines(Data Selector)
- ◆ 4-to-1 multiplexer Diagram : *Fig. 2-4*
- ◆ 4-to-1 multiplexer Function Table : *Tab. 2-3*

*Tab. 2-3 Function Table for
4-to-1 line Multiplexer*

Select		Output
S1	S0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

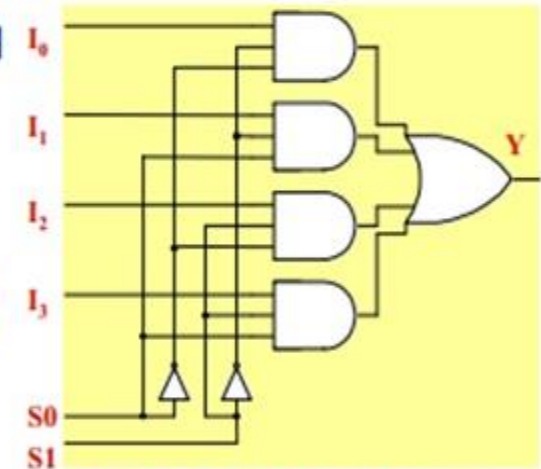


Fig. 2-4 4-to-1 Line Multiplexer


■ Quadruple 2-to-1 Multiplexer

- ◆ Quadruple 2-to-1 Multiplexer : *Fig. 2-5*

*Fig. 2-5 Quadruple 2-to-1
line Multiplexer*

Select		Output
E	S	Y
0	0	All 0's
1	0	A
1	1	B

(a) Function Table

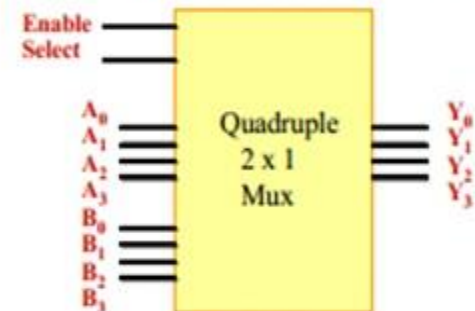

(b) Block Diagram

2-3 Multiplexers


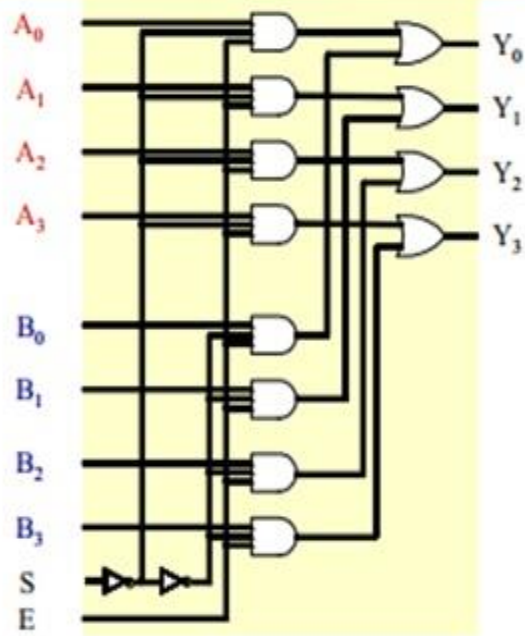


Fig A. Combinational logic diagram with four 2×1 multiplexer

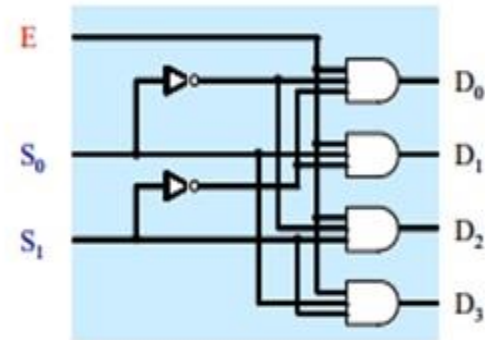

$E \rightarrow$ Data input
 $S_0, S_1 \rightarrow$ Select Data

Fig B. Demultiplexer


A **Demultiplexer**, sometimes abbreviated **DMUX** is a circuit that has one input and more than one output. It is used when a circuit wishes to send a signal to one of many devices

Binary Counters

- It is a hardware circuit in which series of flip-flops are used, to give output of one flip-flop to the input of the next flip-flop.
- Binary counters are used for counting the number of occurrences of an event and are useful for generating timing signals to control the sequence of operations in digital computers.

Binary Counters

- Depending upon the connection setup of flip-flops, binary counters can be either Asynchronous or Synchronous.
- **Asynchronous Counter:** In these, the clock pulses are applied only to the first flip-flop. i.e. all subsequent flip-flops are clocked by the output produced by the preceding flip-flop.
- **Synchronous Counter:** These have a regular pattern i.e. inputs of all flip-flops receive the common clock.

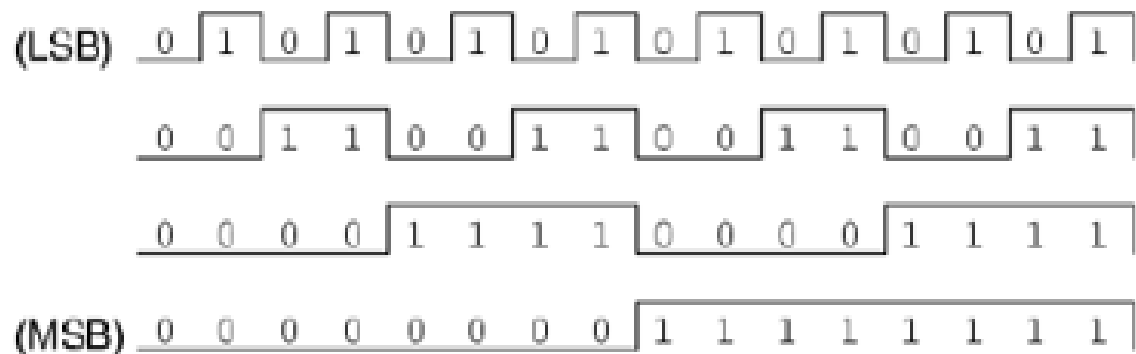

2-4 Registers

■ Register

- ◆ A group of flip-flops with each flip-flop capable of storing one bit of information
- ◆ An n-bit register has a group of n flip-flops and is capable of storing any binary information of n bits
- ◆ The simplest register consists only of flip-flops, with no external gate :

Fig. 2-6

- ◆ A clock input C will load all four inputs in parallel
 - The clock must be *inhibited* if the content of the register must be left unchanged

■ Register with Parallel Load

- ◆ A 4-bit register with a load control input : *Fig. 2-7*
- ◆ The clock inputs receive clock pulses at all times
- ◆ The buffer gate in the clock input will increase “fan-out”
- ◆ Load Input
 - 1 : Four input transfer
 - 0 : Input inhibited, Feedback from output to input(*no change*)

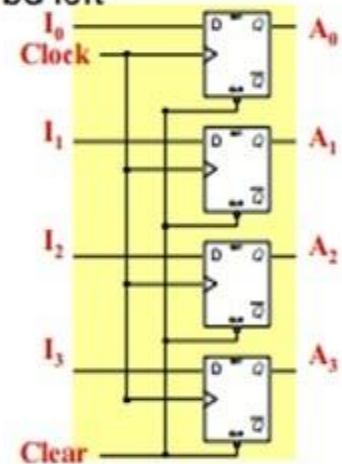


Fig. 2-6 4-bit register

2-4 Registers

- When the load input is 1, the data in the four inputs are transferred into the register with the next positive transition of a clock pulse
- When the load input is 0, the data inputs are inhibited and the D-output of flip flop are connected to their inputs.

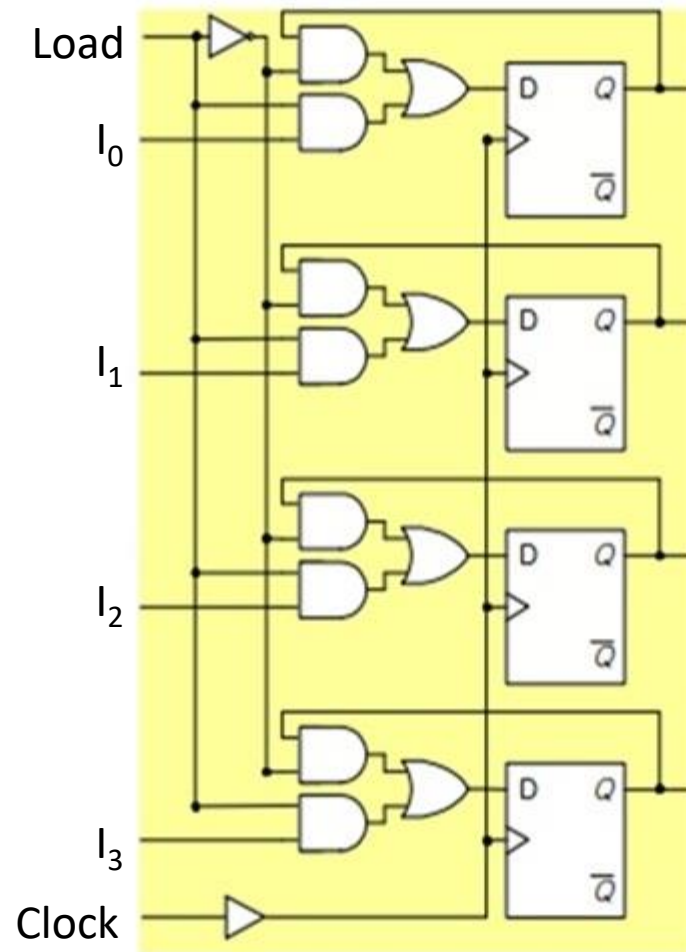


Fig. 2-7 4-bit register with parallel load

2-5 Shift Registers

■ Shift Register

- ◆ A register capable of shifting its binary information in one or both directions
- ◆ The logical configuration of a shift register consists of a chain of flip-flops in cascade
- ◆ The simplest possible shift register uses only flip-flops : *Fig. 2-8*
- ◆ The **serial input** determines what goes into the leftmost position during the shift
- ◆ The **serial output** is taken from the output of the rightmost flip-flop

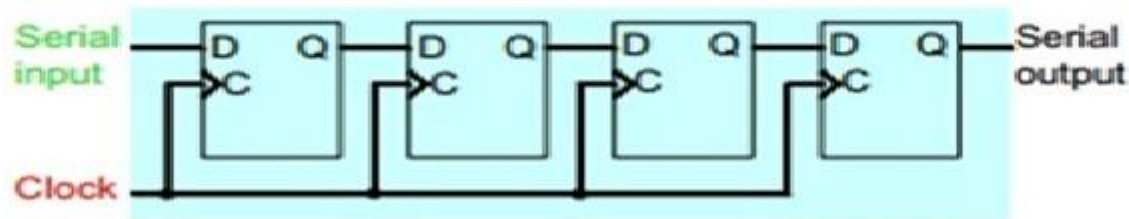


Fig. 2-8 4-bit shift register

2-5 Shift Registers

■ Bidirectional Shift Register with Parallel Load

- ◆ A register capable of shifting in *one direction only* is called a **unidirectional shift register**
- ◆ A register that can shift in *both directions* is called a **bidirectional shift register**
- ◆ The most general shift register has all the capabilities listed below:
 - An input clock pulse to synchronize all operations
 - A shift-right /left (serial output/input)
 - A parallel load, n parallel output lines
 - The register unchanged even though clock pulses are applied continuously
- ◆ 4-bit bidirectional shift register with parallel load :


Fig. 2-9

- 4 X 1 Mux = 4 , D F/F = 4

Tab. 2-4 Function Table for Register of Fig. 2-9

Mode		Operation
S1	S0	
0	0	No change
0	1	Shift right(down)
1	0	shift left(up)
1	1	Parallel load

2-5 Shift Registers

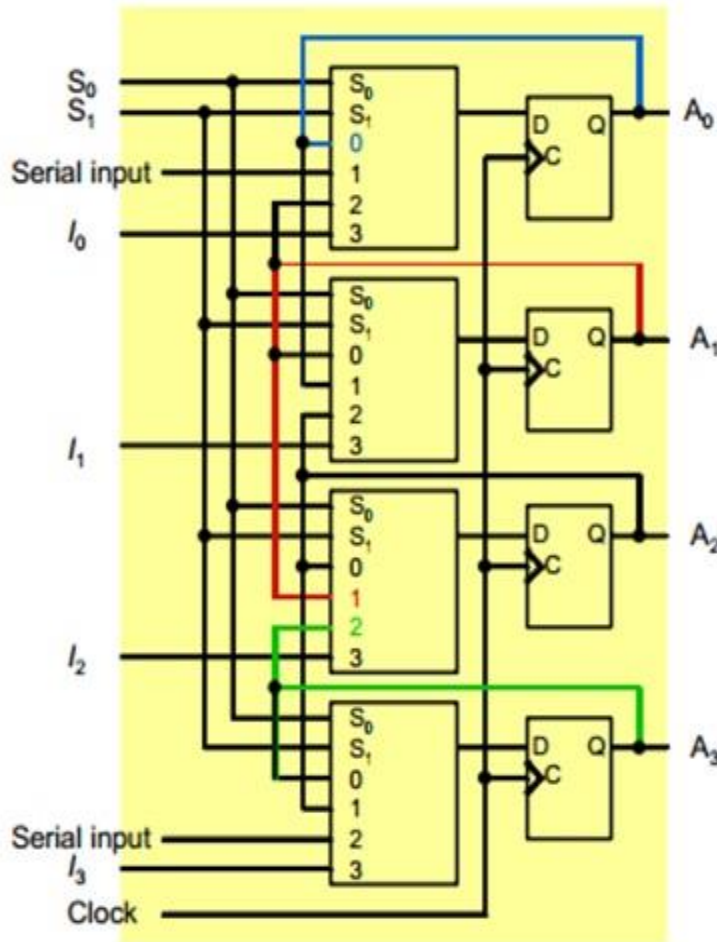

$S_1S_0 = 00$: $A_i \rightarrow A_i$ (No change)

$S_1S_0 = 01$: $A_{i-1} \rightarrow A_i$ (Shift)

$S_1S_0 = 10$: $A_{i+1} \rightarrow A_i$ (Shift)

$S_1S_0 = 11$: Parallel load

■ Shift Register

Interface digital systems situated remotely from each other



Fig. 2-9 Bidirectional shift register