

ECE213: Digital Electronics



Ajmer Singh



9988921373



ajmer.17381@lpu.co.in





The Course Contents

Unit II

Combinational Logic System : Truth table, Basic logic operation, Boolean Algebra, Basic postulates, Standard representation of logic functions -SOP forms, Simplification of switching functions - K-map, Synthesis of combinational logic circuits, Logic gates, Fundamental theorems of Boolean algebra, Standard representation of logic functions POS forms

AB		00	01	11	10
CD	00	0	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	1	1	1




The Course Contents

Unit III

Introduction to Combinational Logic Circuits : Adders, Subtractors, Comparators, Multiplexers and Demultiplexers, Decoders, Encoders, Parity circuits

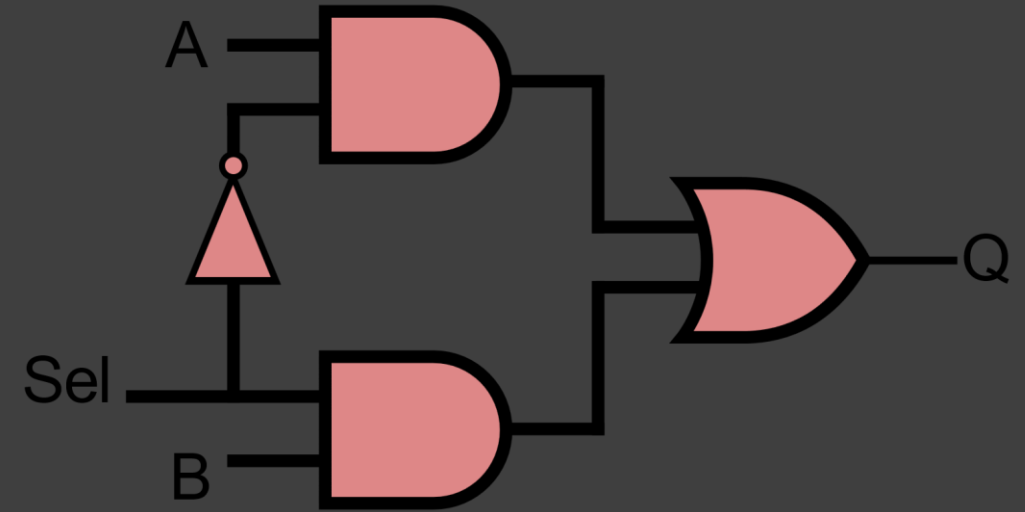
Introduction to Logic Families : Introduction to different logic families, Structure and operations of TTL, MOS and CMOS logic families




Combinational Logic System

Simplification of switching functions - K-map

★ 4-Var K-map

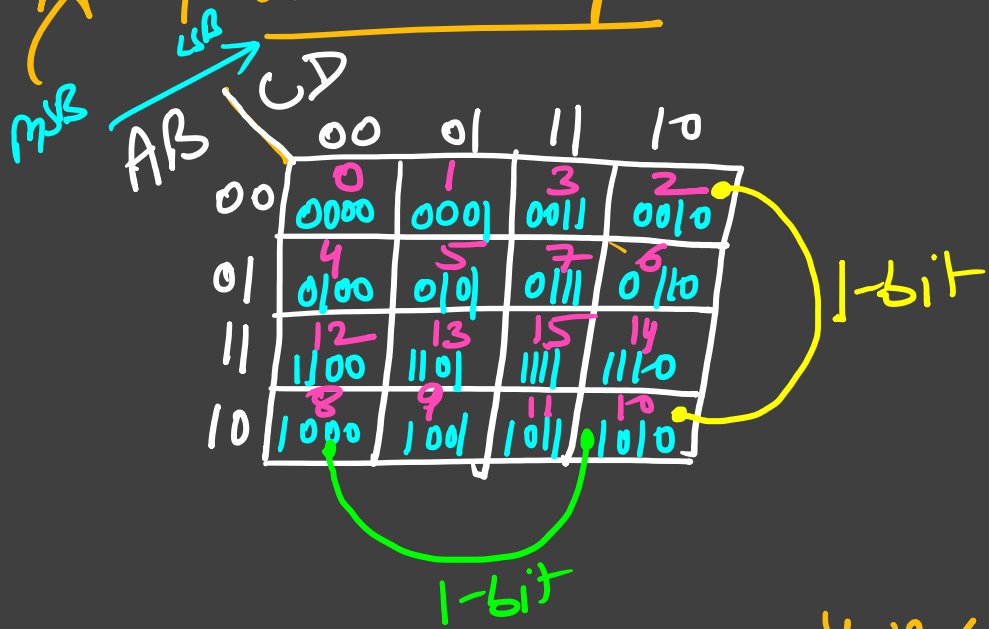



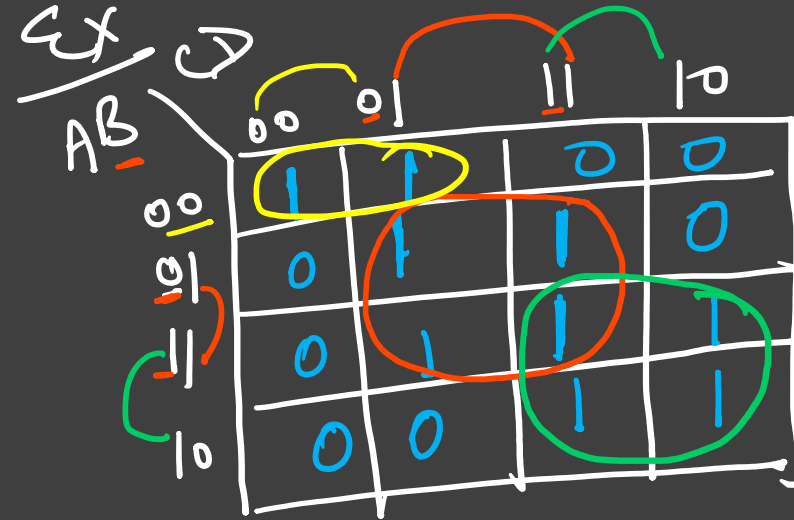
- Possible group size in 4-Var K-map
- 1 cell, 2 cell, 4 cell, 8 cell, 16 cell.



$$Y = BD + AC + \bar{A}\bar{B}\bar{C}$$


Combinational Logic System

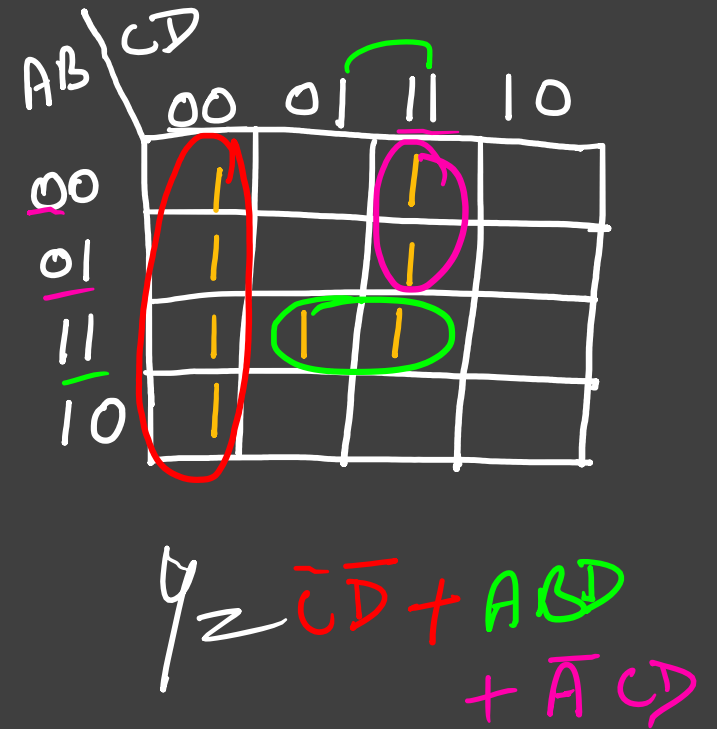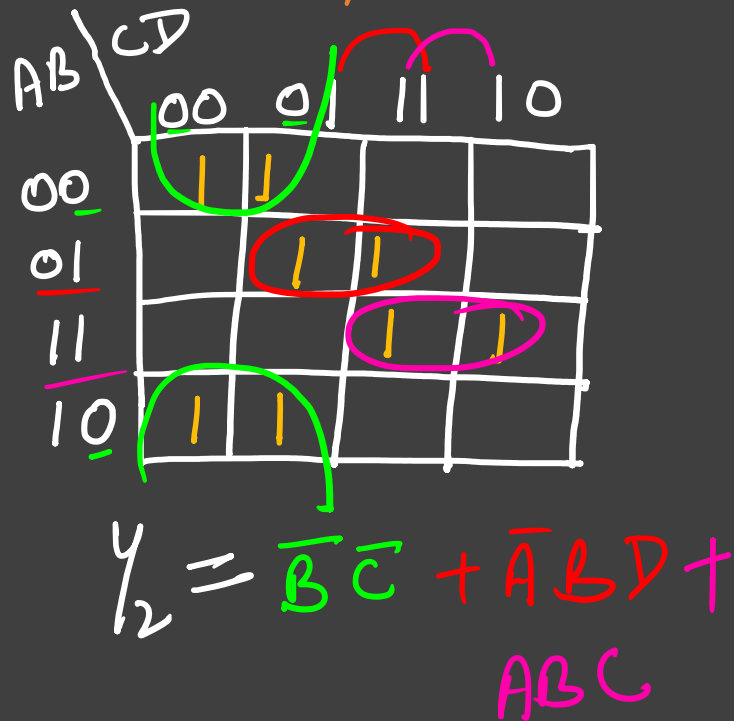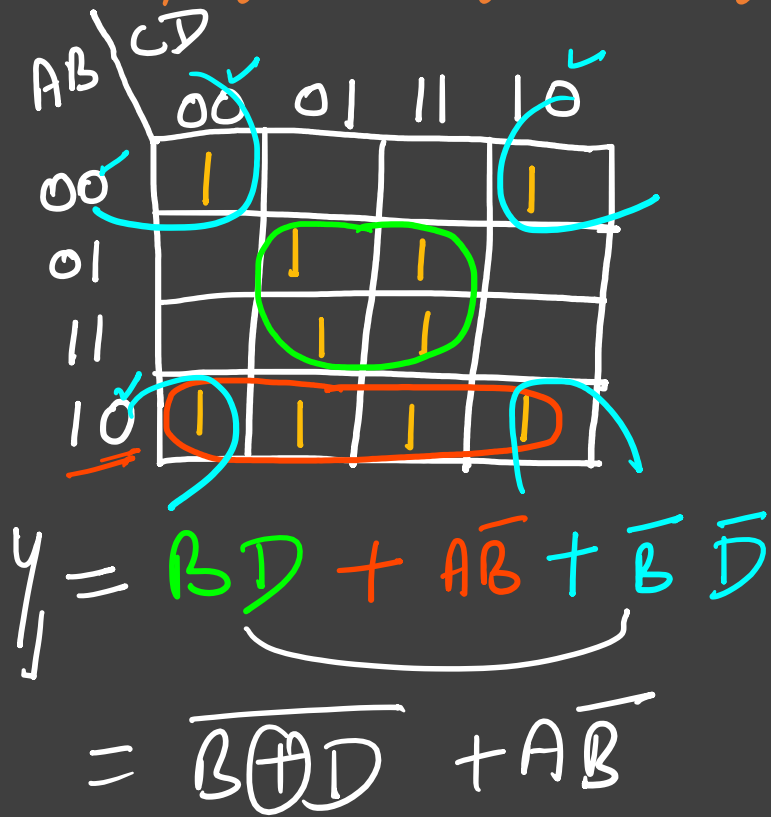Simplification of switching functions - K-map



Combinational Logic System

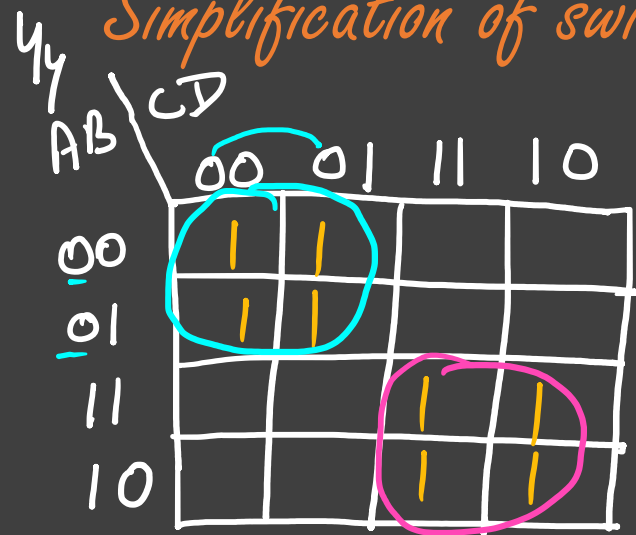Simplification of switching functions - K-map




$$y_4 = \bar{A}\bar{C} + AC$$

$$= \overline{A \oplus C}$$



$$y_5 = \bar{A}\bar{B}C + \bar{A}B\bar{C}$$

$$+ ABC + AB\bar{C}$$

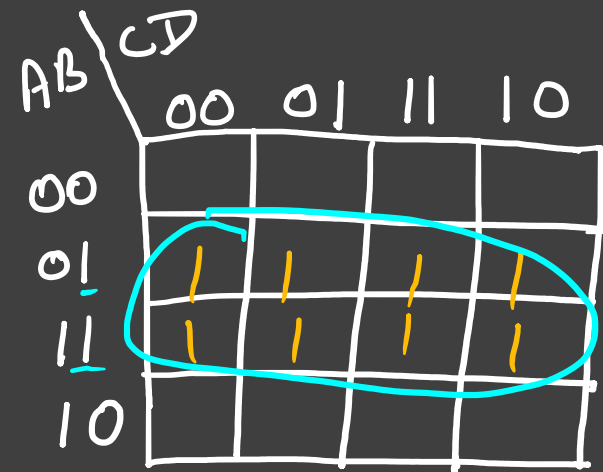

$$y_6 = B$$



Combinational Logic System

Simplification of switching functions - K-map

AB \ CD	00	01	11	10
00	1	1	1	1
01				
11				
10	1	1	1	1

AB \ CD	00	01	11	10
00	1	1	1	1
01	1			1
11	1			1
10	1	1	1	1

AB \ CD	00	01	11	10
00	1	1		
01		1	1	
11			1	1
10				1

Combinational Logic System

Simplification of switching functions - K-map

AB \ CD	00	01	11	10
00		1		
01	1	1	1	1
11	1		1	1
10		1		

AB \ CD	00	01	11	10
00	1			1
01		1	1	1
11	1			
10	1		1	1

AB \ CD	00	01	11	10
00		1		1
01		1		1
11		1		1
10		1		1

Combinational Logic System

Don't Care conditions

Ex

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	X

Don't Care

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	X

$$Y = A\bar{B} \neq$$

A	B	Y
0	0	0
0	1	0
1	0	1
1	1	X

$$Y = A$$

A	B	Y
0	0	0
0	1	X
1	0	1
1	1	X

A	B	Y
0	0	0
0	1	X
1	0	1
1	1	X

~~$$Y = A + B$$~~

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

Noting

$$\bar{A}C + AB = \bar{A}C + AB + BC$$

A	B	Y
0	0	0
0	1	X
1	0	1
1	1	X

$$Y = A$$

Combinational Logic System

Don't Care conditions

Ex: Reduce the boolean fun.

$$Y = \sum m(0, 1, 3, 4) + \underline{d(2)}$$

Sol

A	BC			
	00	01	11	10
0	1	1	1	X
1	1	0	0	0

$$Y = \bar{A} + \bar{B}\bar{C}$$

Combinational Logic System

Don't Care conditions

Ex: Reduce the following function

$$Y = \sum m(\underline{1}, \underline{2}, \underline{4}, \underline{7}, \underline{8}, \underline{10}, \underline{11}, \underline{12}) + d(\underline{3}, \underline{9}, \underline{15})$$

AB \ CD				
	00	01	11	10
00	0	1	1	1
01	1	0	1	0
11	1	0	1	0
10	1	1	1	1

$$Y = \underline{CD} + \underline{A\bar{B}} + \underline{B\bar{C}\bar{D}} + \underline{\bar{A}\bar{B}C} + \underline{\bar{A}\bar{B}D}$$

Combinational Logic System

Don't Care conditions

Ex Reduce the following function

$$Y = \prod M(\underline{0}, \underline{1}, \underline{5}, \underline{8}, 9, 12) \cdot d(2, 3, 14, 15)$$

AB \ CD				
	00	01	11	10
00	0	0	X	X
01	1	0	1	1
11	0	1	X	X
10	0	0	1	1

$$Y = C + ABD + \bar{A}B\bar{D}$$

Unit 3 Combinational Logic System

2-bit Comparator

1-bit

A	B	Y_1 $A=B$	Y_2 $A > B$	Y_3 $A < B$
0	0	1	0	0
0	1	0	0	1
1	0	0	1	0
1	1	1	0	0

for Y_1

A	B
0	0
1	1

$$Y_1 = \overline{A}\overline{B} + AB = \overline{A \oplus B}$$

for Y_2


A	B
0	1
1	0

$$Y_2 = A\overline{B}$$

for Y_3

A	B
1	0
0	1

$$Y_3 = \overline{A}B$$

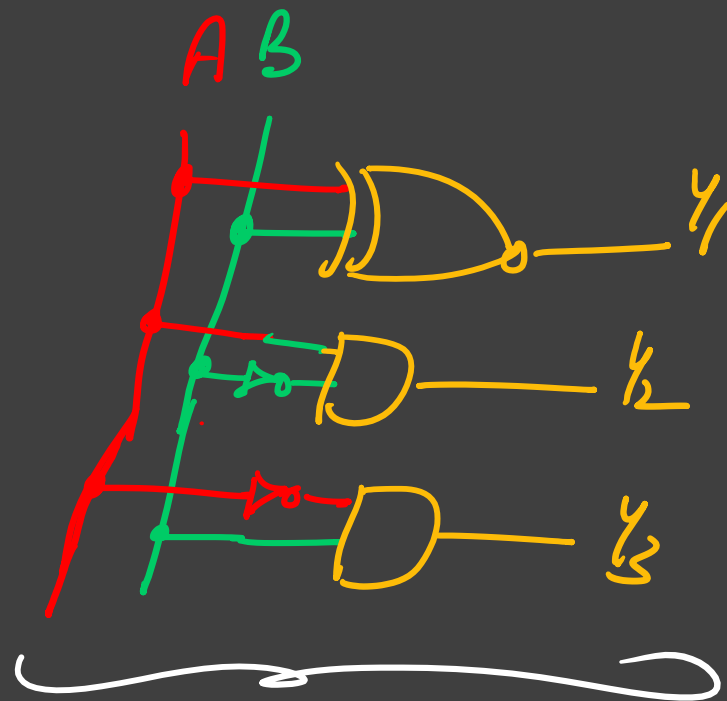

1-bit Comparators

Combinational Logic System

2-bit Comparator

A		B		y_1	y_2	y_3
A_1	A_0	B_1	B_0	$A=B$	$A>B$	$A<B$
0	0	0	0	1	0	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	0	1	0
0	1	0	1	0	0	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	0	1	0
1	0	0	1	0	0	0
1	0	1	0	0	0	0
1	0	1	1	0	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	0	1

for y_1

$A_1 A_0$	$B_1 B_0$	00	01	11	10
00	00	1	0	0	0
01	00	0	1	0	0
11	00	0	0	1	0
10	00	0	0	0	1

$$\begin{aligned}
 y_1 &= \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 \\
 &\quad + \bar{A}_1 A_0 \bar{B}_1 B_0 \\
 &\quad + A_1 A_0 B_1 B_0 \\
 &\quad + A_1 \bar{A}_0 B_1 \bar{B}_0 \\
 &= \bar{A}_1 \bar{B}_1 (\bar{A}_0 \bar{B}_0 + A_0 B_0) \\
 &\quad + A_1 B_1 (\bar{A}_0 \bar{B}_0 + A_0 B_0) \\
 &= \overline{A_0 \oplus B_0} (\bar{A}_1 \bar{B}_1 + A_1 B_1) \\
 &= \overline{A_0 + B_0} \cdot \overline{A_1 \oplus B_1}
 \end{aligned}$$

for y_2

$A_1 A_0$	$B_1 B_0$	00	01	11	10
00	00	0	0	0	0
01	00	1	0	0	0
11	00	1	1	0	1
10	00	1	1	0	0

$$\begin{aligned}
 y_2 &= A_1 \bar{B}_1 + A_0 \bar{B}_1 \bar{B}_0 \\
 &\quad + A_1 A_0 \bar{B}_0
 \end{aligned}$$

for y_3 (H.W)

$A_1 A_0$	$B_1 B_0$	00	01	11	10
00	00	0	1	1	1
01	00	0	0	1	1
11	00	0	0	0	0
10	00	0	0	1	0

$$\begin{aligned}
 y_3 &= \bar{A}_1 B_1 + \bar{A}_1 \bar{A}_0 B_0 + \bar{A}_0 B_1 B_0
 \end{aligned}$$



Combinational Logic System

2-bit Comparator

cat day (7/14)