

- 1) Name the filter that has two stop bands?
a) **Band-pass filter**
b) Low pass filter
c) High pass filter
d) Band-reject filter
- 2) In a certain low-pass filter, $f_c = 5$ kHz. Its pass band is
(A) 0 Hz
(B) **0 Hz to 5 kHz**
(C) 9 kHz
(D) 4.5 kHz
- 3) Which filter performs exactly the opposite to the band-pass filter?
a) Band-reject filter
b) Band-stop filter
c) Band-elimination filter
d) **All of the mentioned**
- 4) What is a filter?
a) **Frequency selective circuit**
b) Amplitude selective circuit
c) Frequency damping circuit
d) Amplitude damping circuit
- 5) What are filters created by using resistors and capacitors or inductors and capacitors called?
a) Active filters
b) **Passive filters**
c) Continuous filters
d) Differential filters
- 6) Find the cut off frequency for an RC low pass filter of $R=8.2$ k Ω and $C=0.0022\mu\text{F}$?
a) 6KHz
b) **8.82 KHz**
c) 7.72 KHz
d) 7.91KHz
- 7) What is the value of resistor for a high pass RC filter to produce a cutoff frequency of 3.4KHz if $C = 0.037\mu\text{F}$?
a) 1295
b) **1265**
c) 1285
d) 1245
- 8) An RC low-pass filter consists of a 100 resistor and a 0.001 F capacitor. The output is taken across the capacitor. The circuit's critical frequency is
A. 1.59 Hz

- B. 1.69 Hz
- C. 1.79 Hz
- D. 1.89 Hz

9) A certain noninverting amplifier has R_i of 1 k Ω and R_f of 101 k Ω . The closed-loop voltage gain is

- A) 10000
- B) 100
- C) 102
- D) 1000

10) Current cannot flow to ground through

- A) a mechanical ground
- B) an a.c. ground
- C) a virtual ground
- D) an ordinary ground

11) How will be the output voltage obtained for an ideal op-amp?

- a) Amplifies the difference between the two input voltages
- b) Amplifies individual voltages input voltages
- c) Amplifies products of two input voltage
- d) None of the mentioned

12) Find the input voltage of an ideal op-amp. It's one of the inputs and output voltages are 2v and 12v. (Gain=3)

- a) 8v
- b) 4v
- c) -4v
- d) -2v

13) Op-amps used as high- and low-pass filter circuits employ which configuration?

- A. noninverting
- B. comparator
- C. open-loop
- D. inverting

14) Which concept states that if one input terminal of an op-amp is at zero potential, then the other one also will be at zero potential?

- a. Virtual short
- b. Virtual ground
- c. Zero input current
- d. None of the above

15) The output voltage of an open-loop differential amplifier is equal to

- a) Double the difference between the two input voltages
- b) Product of voltage gain and individual input voltages
- c) Product of voltage gain and the difference between the two input voltages
- d) Double the voltage gain and the difference between two input voltages

16) For an Op-amp with negative feedback, the output is

- A) equal to the input
- B) increased
- C) fed back to the inverting input
- D) fed back to the noninverting input

17) The two input terminals of an opamp are labeled as

- A) High and low
- B) Positive and negative
- C) Inverting and non inverting
- D) Differential and non differential

18) Which statement is true in view of micro controller

- A) microcontroller consists of the processor, the memory, Serial ports, peripherals
- B) A microcontroller is a small and low-cost microcomputer
- C) It is designed to perform the specific tasks of embedded systems
- D) All of the above

19) A microcontroller consist of:

- a) RAM, ROM, I/O ports and timers
- b) CPU, RAM, I/O ports and timers
- c) CPU, RAM, ROM, I/O ports and timers
- d) CPU, ROM, I/O ports and timers

20) A microprocessor is a Chip integrating all the functions of a CPU of a computer

- A) Single
- B) Multiple
- C) Double
- D) Triple

21) Micro processor is the of the computer and it perform all the computational tasks

- A) Main
- B) Brain
- C) Heart
- D) Important

22) ASIC stands for

- A) Application Specific Integrated Circuits
- B) Application sorted integrated circuits
- C) Application solution integrated circuit
- D) Application specific input circuit

23) Applications of digital signal processor

- A) Speech processing
- B) Image processing
- C) Medical processing
- D) All of the above

24) In which OS large memory is required

- A) RTOS
- B) GPOS
- C) Both
- D) None of the above

25) Which platforms are the example of GPOS

- A) Linux
- B) Windows
- C) Mac OS
- D) All of the above

26) FPGA contains

- A) Adders
- B) multipliers
- C) Both
- D) Neither adders nor multipliers

27) 80186 is a

- A) 8 bit processor
- B) 16 bit processor
- C) 32 bit processor
- D) 64 bit processor

28) Components of embedded system

- A) Only hardware
- B) application software
- C) OS
- D) All of the above

29) These devices provide a means of communication between a computer and outer world

- a) I/O
- b) Storage
- c) Compact
- d) Drivers

30) Among the options which of the following computer input device enable video conference?

- A) Microphone
- B) Digital Camera
- C) Voice recognition
- D) Webcam

The power rating of a BJT is determined by which of the following

- A. Collector base area
- B. Base width
- C. Heat sink
- D. Emitter base junction area

In CB configuration, a transistor transfers

- ✦ Voltage from high impedance circuit to low impedance
- ✦ Voltage from low impedance circuit to high impedance
- ✦ Current from high impedance circuit to low impedance circuit
- ✦ Current from low impedance circuit to high impedance circuit

When a transistor is in active region in CB configuration, the resistance is high between

- ✦ Emitter to collector
- ✦ Base to collector
- ✦ Emitter to base
- ✦ All of the above

A transistor is said to be operating in the cut-off region if

- ✦ Emitter junction is forward biased and collector junction is forward biased
- ✦ Emitter junction is reverse biased and collector junction is forward biased
- ✦ Emitter junction is forward biased and collector junction is reverse biased
- ✦ Emitter junction is reverse biased and collector junction is reverse biased

MOSFET has greatest application in digital circuit due to

- ✦ Low power consumption
- ✦ Less noise
- ✦ Small amount of space it takes on a chip
- ✦ All of the above

The depletion region of the Zener diode is _____

- ✦ very thick
- ✦ very thin
- ✦ thick

- ✦ Normal

In the breakdown region, a zener diode behaves like a source.

- ✦ Constant current
- ✦ constant voltage
- ✦ constant resistance
- ✦ none of the above

In N-channel Enhancement MOSFET, for inversion the gate to source voltage (V_{GS}) is

- ✦ less than 0
- ✦ greater than 0
- ✦ is equal to drain voltage
- ✦ None of the above

An N-Channel depletion MOSFET, when gate source voltage (V_{GS}) is extremely negative, then the status of channel is

- ✦ depletion of electrons
- ✦ Accumulation of electrons
- ✦ depletion of holes
- ✦ none of the above

FPGA devices are _____ type.

- ✦ PLD
- ✦ EPROM
- ✦ SPROM
- ✦ None of the above

Which of the following are correct characteristics of RISC?

- ✦ It supports register to use in any context.
- ✦ It consists of simple instructions.
- ✦ It supports various data-type formats.
- ✦ All of the above

Which of the following are incorrect characteristics of CISC?

- ♦ Variety of addressing modes.
- ♦ Variable length of instruction format
- ♦ Instruction-decoding logic is complex.

♦ Small number of instructions.

Which among following statement/s is NOT correct related to IoT in healthcare.

- A. efficient autonomous systems will cost less to manage and 'employ' in the long run.
- B. Doctors can view all the necessary data on command and check real-time patient conditions without leaving their office
- C. Privacy cannot be potentially undermined
- D. Wearables contains less health tracking features and continue down in the market.

♦ B & D

♦ C & D

♦ A & D

♦ A & B

What is the role of Cloud in smart grid architecture of IoT?

♦ Store data

♦ Manage data

♦ Collect data

♦ Security

Which among statements are true for microcontroller

- A. The MCU is application-specific i.e. it is designed for performing a single specific task.
- B. Its processing speed is 8Mhz to 50Mhz. thus it cannot be used for complex tasks.
- C. It has an internal fixed amount of memory that cannot be upgraded.
- D. It needs external components thus the devices made it are bulkier
- E. It is the central processing unit of the computer

♦ A & B & D

♦ A & B & C

♦ A & C & E

♦ B & D & E

What is the Propagation delay?

- ♦ the time taken for the output of a gate to change after the intermediates have changed
- ♦ the time taken for the input of a gate to change after the intermediates have changed
- ♦ the time taken for the input of a gate to change after the outputs have changed
- ♦ the time taken for the output of a gate to change after the inputs have changed

What is the maximum noise voltage that may appear at the input of a logic gate without changing the logical state of its output is termed as _____

- ◆ Noise Immunity
- ◆ Noise Margin
- ◆ White Noise
- ◆ None of the these