

# ECE213: Digital Electronics





Ajmer Singh



9988921373



ajmer.17381@lpu.co.in

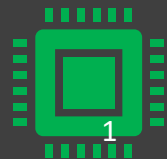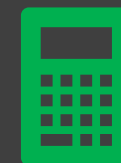




# The Course Contents

## Unit IV

★ Introduction to Sequential Logic Circuits : Basic  
sequential circuits: SR-latch, D-latch, D flipflop, JK  
flip-flop, T flip-flop, Conversion of basic flip-flops



# Next o/p depends on the prev. o/p.

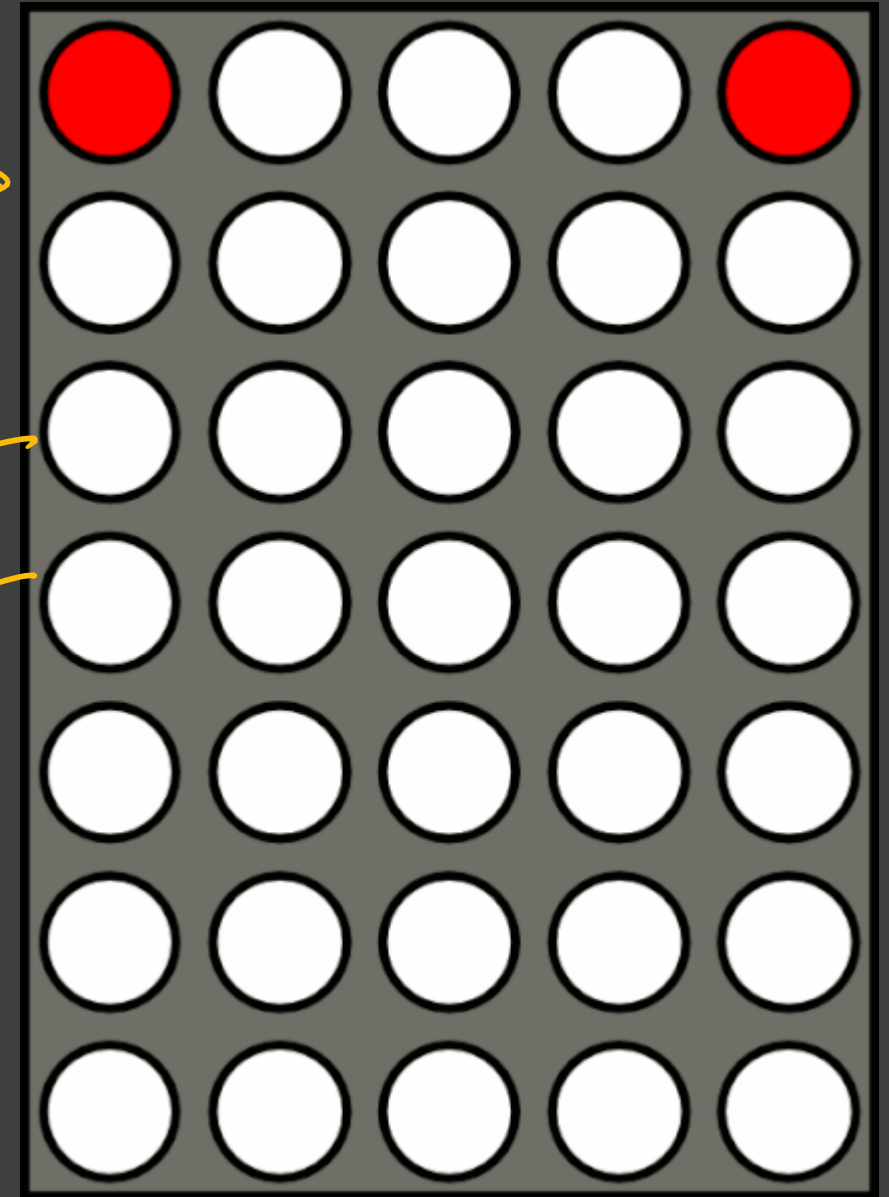

# Introduction to Sequential Logic Circuits

## Sequential Logic Circuits

⇒ Combinational Logic      Sequential

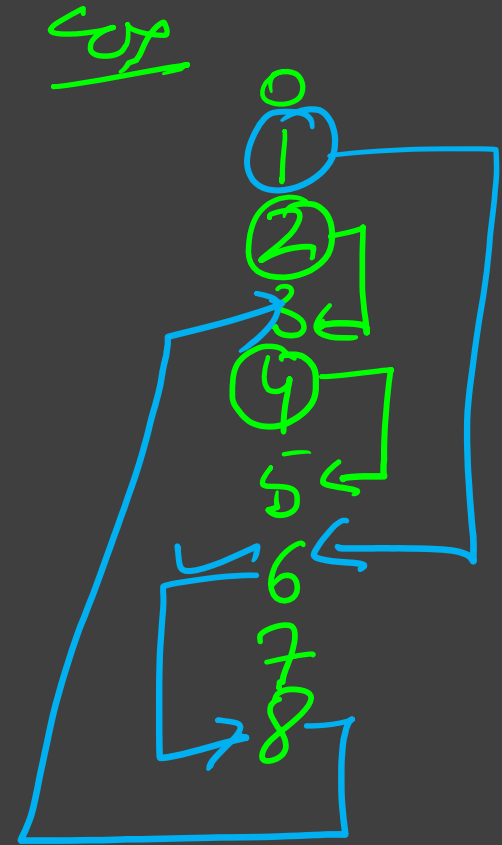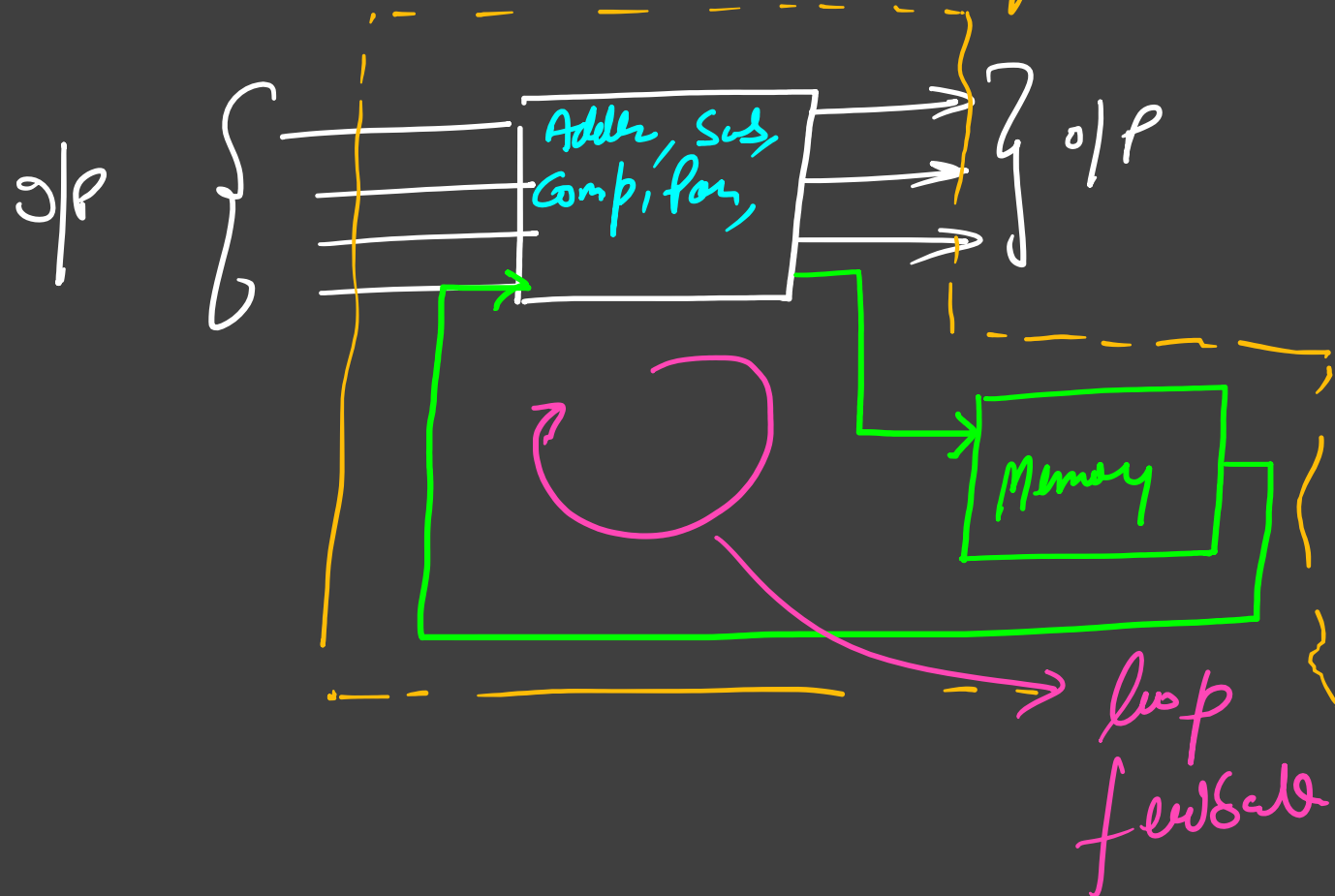


# Introduction to Sequential Logic Circuits

## Sequential Logic Circuits

	Combinational Circuit	Sequential Circuit
Definition	Combinational Circuit is the type of circuit in which output is <u>independent of time</u> and only relies on the <u>input present</u> at that particular instant.	On other hand Sequential circuit is the type of circuit where output not only relies on the <u>current input</u> but also <u>depends on the previous output</u> .
Feedback	In Combinational circuit as <u>output</u> does not depend on the <u>time</u> instant, <u>no feedback</u> is required for its next output generation.	On other hand in case of Sequential circuit output relies on its previous <u>feedback</u> so output of previous input is being transferred as feedback used with input for next output generation.
Performance	As the input of current instant is only required in case of Combinational circuit, it is <u>faster</u> and better in performance as compared to that of Sequential circuit.	On other hand Sequential circuit are comparatively <u>slower</u> and has <u>low performance</u> as compared to that of Combinational circuit.
Complexity	No implementation of feedback makes the combinational circuit <u>less complex</u> as compared to sequential circuit.	However on other hand implementation of feedback makes sequential circuit <u>more complex</u> as compared to combinational circuit.
Elementary Blocks	Elementary building blocks for combinational circuit are <u>logic gates</u> .	On other hand building blocks for sequential circuit are <u>flip flops</u> . <i>If can store one bit data.</i>
Operation	Combinational circuit are mainly used for <u>arithmetic</u> as well as Boolean operations.	On other hand Sequential circuit is mainly used for <u>storing data</u> .


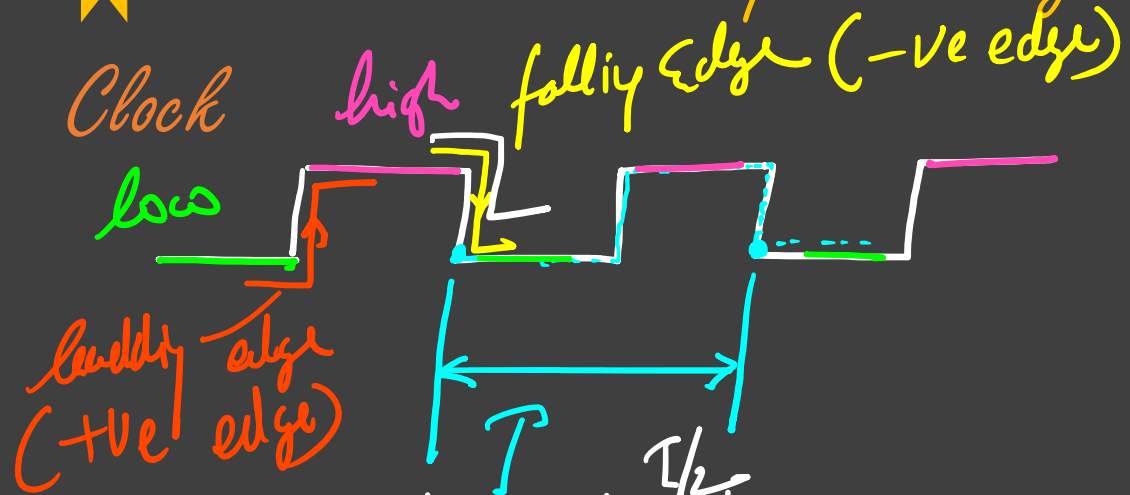
# Introduction to Sequential Logic Circuits




- # low level (-ve level)
- # high level (+ve level)
- # leading edge (+ve edge)
- # falling edge (-ve edge)

✓ Time/period ( $T$ ) time to complete one cycle

✓ Frequency ( $f$ ) No. of cycles in one unit time

$$f = \frac{1}{T}$$

Ex

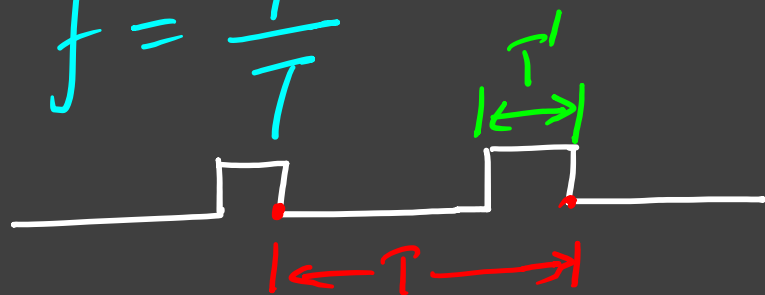

$$D.C = \frac{T'}{T}$$






★ Duty Cycle : Ratio of time for high level to time per.

$$D.C = \frac{T/2}{T} = 50\%$$

# Introduction to Sequential Logic Circuits


## ★ Triggering Methods

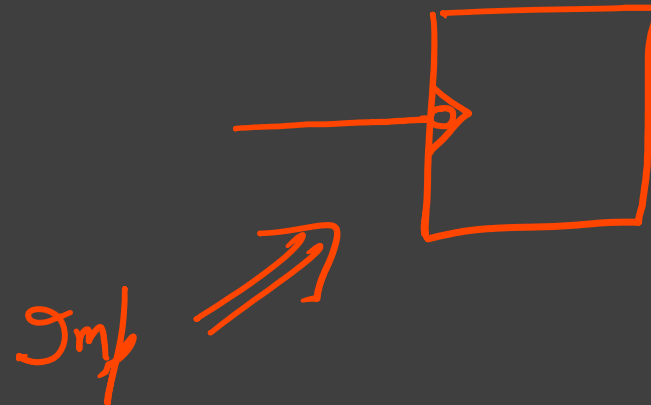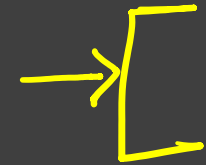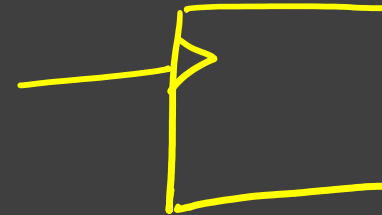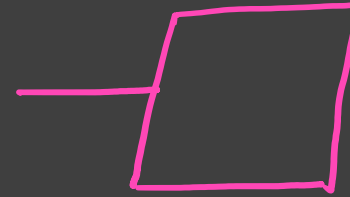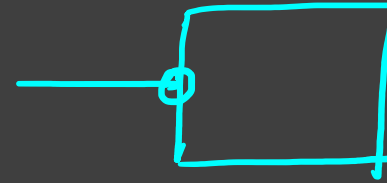- 1) -ve level triggering]
- 2) +ve level triggering]
- 3) +ve edge triggering]
- 4) -ve edge trigger]


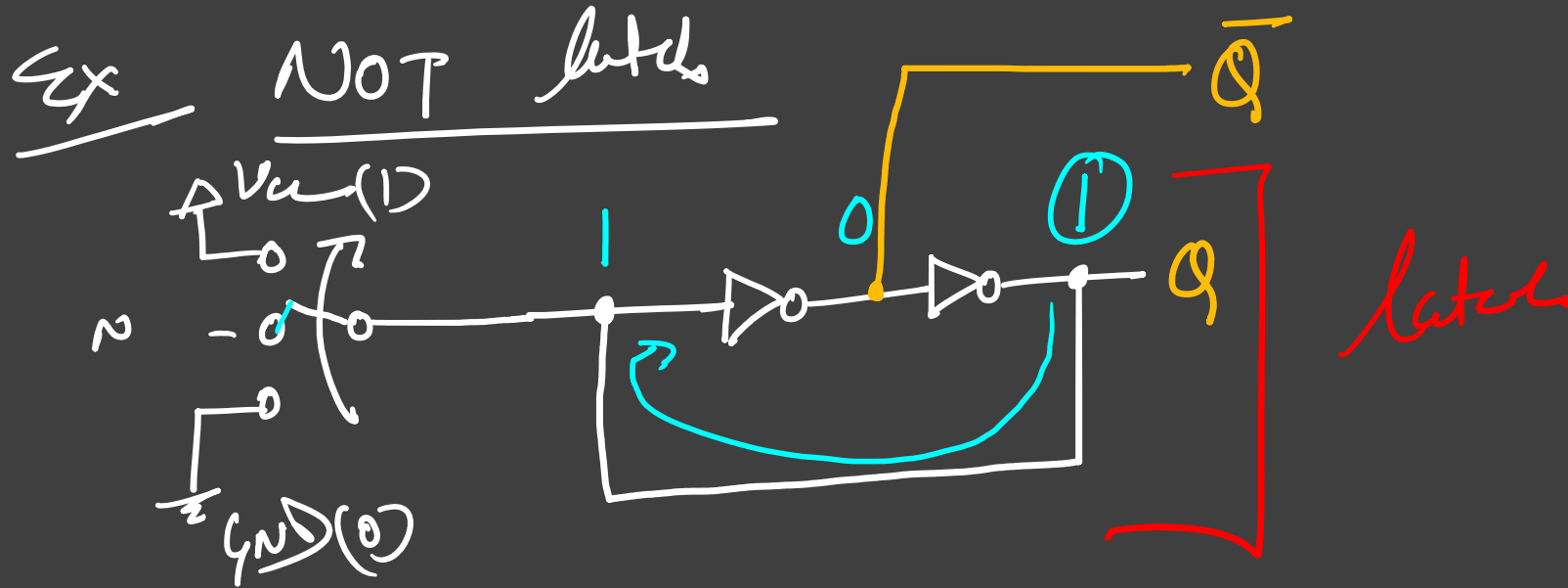
# Introduction to Sequential Logic Circuits

★ Latch : It can store 1-bit data  
It is a kind of loop (feedback)



# Introduction to Sequential Logic Circuits

## SR Latch (NOR)

Set      Reset

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	-	-


Reset      Set

Case 1: If  $S=0, R=0$ , No change Condition (Memory)

Case 2: If  $S=0, R=1$ , Reset Condition

Case 3: If  $S=1, R=0$ , Set Condition

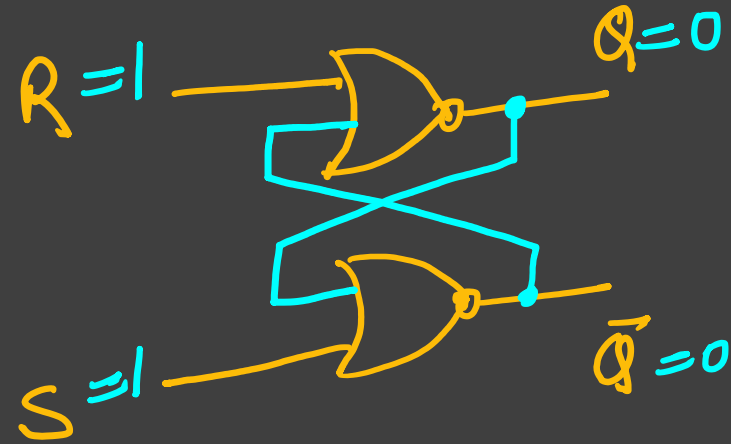Case 4: If  $S=1, R=1$ , Invalid Condition  
 $Q = \bar{Q}$  (Invalid)



\* NOR Logic

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

Set Condition: When the o/p of the circuit set to high, irrespective of previous o/p.

Reset Condition: When the o/p of the circuit set to low, irrespective of previous o/p.

✓ 1) If any of the i/p is high then o/p is low.

✓ 2) If any of the i/p is low, then the o/p is the complement of 2<sup>nd</sup> input.