

Pre Lab Worksheet (Exp 10)

Question 1: Calculate the current through the zener diode and the voltage across the Rload resistance for the given circuit. If the Rload (k Ohm) is the last two digits of your roll number (Example: for the Roll number: REX124A15 Rload is 15 kOhm)

