

# Combinational Circuits

- It is a connected arrangement of logic gates with a set of inputs and outputs.
- Combinational circuits are employed in digital computers for generating binary control decisions and for providing digital components required for data processing. HALF ADDER and FULL ADDER


# Combinational Circuits

- No feedback paths
- No memory
- Combinational circuit is a connected arrangement of logic gates with set of inputs and outputs.
- Binary values of outputs are a function of binary combination of inputs.

# Combinational Circuits

- In this, output depends only upon present input.
- Speed is fast.
- It is designed easy.
- There is no feedback between input and output.
- This is time independent.
- Elementary building blocks: Logic gates
- Used for arithmetic as well as boolean operations.
- Combinational circuits don't have capability to store any state.
- As combinational circuits don't have clock, they don't require triggering.
- These circuits do not have any memory element.
- It is easy to use and handle.

## Block Diagram -

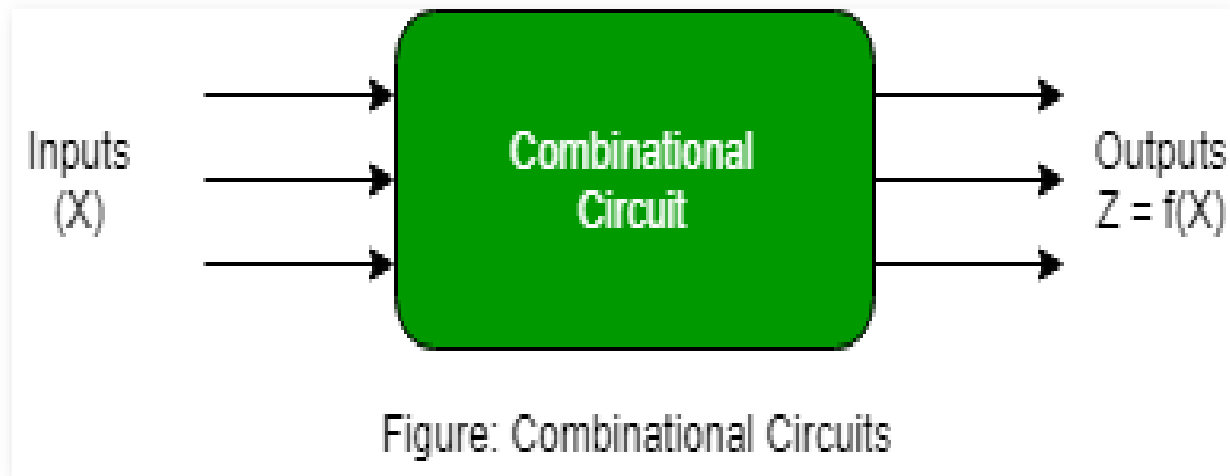


# HALF ADDER

- Performs arithmetic addition of two bits.
- Input variables are called as AUGEND and ADDEND
- Output Variables are SUM and CARRY

| $x$ | $y$ | $C$ | $S$ |
|-----|-----|-----|-----|
| 0   | 0   | 0   | 0   |
| 0   | 1   | 0   | 1   |
| 1   | 0   | 0   | 1   |
| 1   | 1   | 1   | 0   |

(a) Truth table

 

(b) Logic diagram

$$S = x'y + xy' = x \oplus y$$

$$C = xy$$

Figure 1-16 Half-adder.

# FULL ADDER

- Performs arithmetic addition of three bits.
- Consists of three inputs and two outputs.

TABLE 1-2 Truth Table for Full-Adder


| Inputs |     |     | Outputs |     |
|--------|-----|-----|---------|-----|
| $x$    | $y$ | $z$ | $C$     | $S$ |
| 0      | 0   | 0   | 0       | 0   |
| 0      | 0   | 1   | 0       | 1   |
| 0      | 1   | 0   | 0       | 1   |
| 0      | 1   | 1   | 1       | 0   |
| 1      | 0   | 0   | 0       | 1   |
| 1      | 0   | 1   | 1       | 0   |
| 1      | 1   | 0   | 1       | 0   |
| 1      | 1   | 1   | 1       | 1   |

# FULL ADDER


$$S = x \oplus y \oplus z$$

$$C = xy + (x \oplus y)z$$

$$C = xy + (x'y + xy')z$$

 

(a) Logic diagram

 

(b) Block diagram

Figure 1-18 Full-adder circuit.

# Sequential Circuits

- Feedback paths exist
- Memory present
- 2 Types- Synchronous and Asynchronous
- Synchronous sequential circuits employ signals that effect storage elements only at discrete instants of time.
- Synchronization is achieved with help of device called clock.



# Sequential Circuits


- **Asynchronous sequential logic** is not **synchronized** by a clock signal; the outputs of the **circuit** change directly in response to changes in inputs. The advantage of **asynchronous logic** is that it can be faster than **synchronous logic**, because the **circuit** doesn't have to wait for a clock signal to process inputs.

# Sequential circuits

- **Sequential circuits** are those which are dependent on clock cycles and depends on present as well as past inputs to generate any output.

Block Diagram –

Examples – Flip-flops, Counters

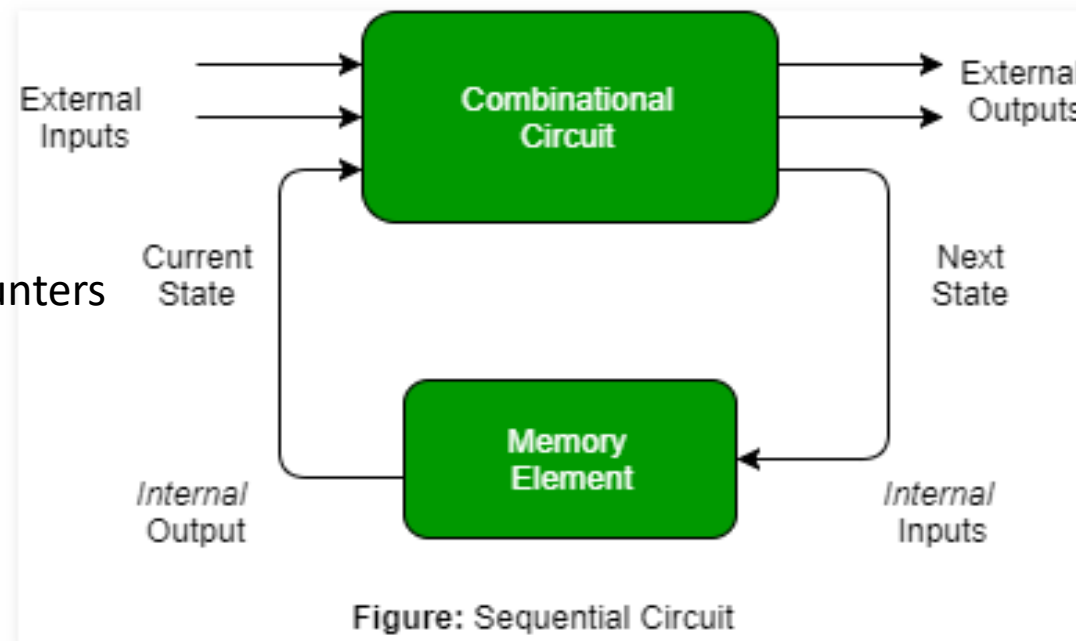

# Sequential Circuit

- In this output depends upon present as well as past input.
- Speed is slow.
- It is designed tough as compared to combinational circuits.
- There exists a feedback path between input and output.
- This is time dependent.
- Elementary building blocks: Flip-flops
- Mainly used for storing data.
- Sequential circuits have capability to store any state or to retain earlier state.
- As sequential circuits are clock dependent they need triggering.
- These circuits have memory element.
- It is not easy to use and handle.


# 1-6 Flip-Flops

Combinational Circuit = Gate  
Sequential Circuit = Gate + F/F

## ■ Flip-Flop


- ◆ The *storage elements* employed in clocked *sequential circuit*
- ◆ A binary cell capable of storing one bit of information

## ■ SR(*Set/Reset*) F/F

 

| S | R | Q(t) | Q(t+1)        |
|---|---|------|---------------|
| 0 | 0 | Q(t) | no change     |
| 0 | 1 | 0    | clear to 0    |
| 1 | 0 | 1    | set to 1      |
| 1 | 1 | ?    | Indeterminate |

## ■ D(*Data*) F/F

 


| D | Q(t) | Q(t+1)     |
|---|------|------------|
| 0 | 0    | clear to 0 |
| 1 | 1    | set to 1   |

- ◆ "no change" condition

- 1) Disable Clock
- 2) Feedback output into input


## ■ JK(*Jack/King*) F/F

 

| J | K | Q(t) | Q(t+1)     |
|---|---|------|------------|
| 0 | 0 | Q(t) | no change  |
| 0 | 1 | 0    | clear to 0 |
| 1 | 0 | 1    | set to 1   |
| 1 | 1 | Q(t) | Complement |

- ◆ JK F/F is a refinement of the SR F/F
- ◆ The indeterminate condition of the SR type is defined in complement

## ■ T(*Toggle*) F/F

 


| T | Q(t) | Q(t+1)           |
|---|------|------------------|
| 0 | Q(t) | no change        |
| 1 | Q(t) | Q'(t) Complement |


- ◆  $T=1(J=K=1)$ ,  $T=0(J=K=0)$

## 1-6 Flip-Flops


### ■ SR(*Set/Reset*) F/F

 


### ■ D(*Data*) F/F

 

### ■ JK(*Jack/King*) F/F



 


### ■ T(*Toggle*) F/F

 

## 1-6 Flip-Flops

### ■ Master – Slave D(Data) F/F

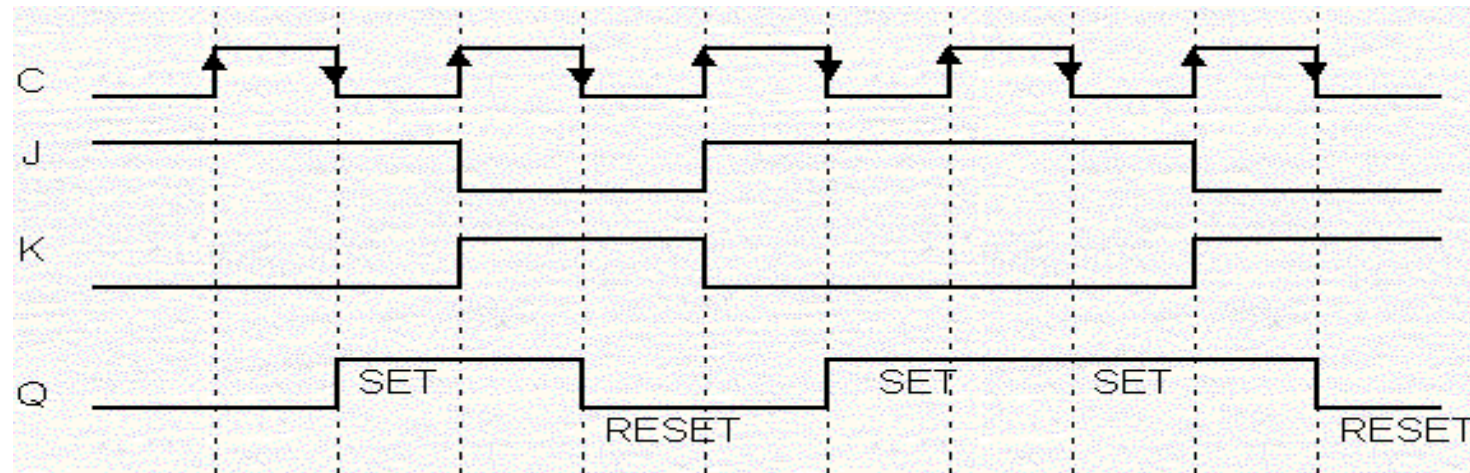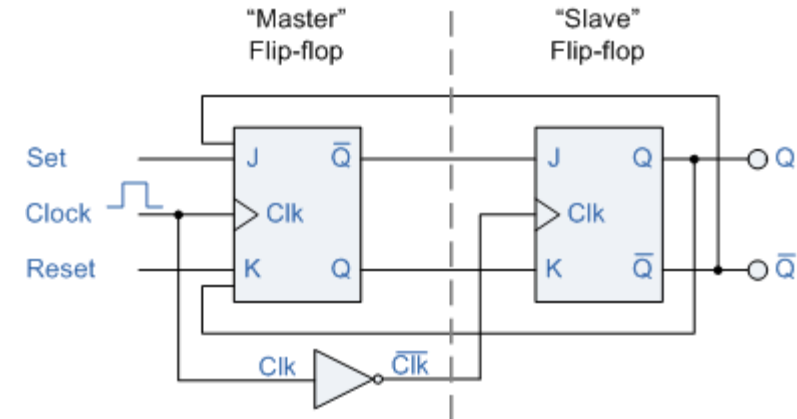 






## 1-6 Flip-Flops

### ■ Edge-Triggered F/F
 
#### ◆ State Change : *Clock Pulse*

- Rising Edge(positive-edge transition) 
- Falling Edge(negative-edge transition) 



#### ◆ Setup time(20ns)

- minimum time that D input must remain at constant value before the transition.

#### ◆ Hold time(5ns)

- minimum time that D input must not change after the positive transition.

#### ◆ Propagation delay(max 50ns)

- time between the clock input and the response in Q

#### ◆ Master-Slave F/F

**Master Slave flip flop** are the cascaded combination of two flip-flops among which the first is designated as master flip-flop while the next is called slave flip-flop

An IC is a small silicon semiconductor crystal called chip containing the electronic components for digital gates.

- Various gates are interconnected inside chip to form required circuit.
- Chip is mounted in ceramic/plastic container connected to external pin

**Small scale Integration (SSI)** : less than 10 gates

**Medium Scale Integration(MSI)** : between 10 to 200 gates  
(decoders, adders, registers)

**Large Scale Integration(LSI)** : between 200 and few thousands gates  
( Processors, Memory Chips)

**Very Large Scale Integration (VLSI)** : Thousands of gate within  
single package ( Large Memory Arrays, Complex Microcomputer Chips)



