


# FLIP FLOP

Combinational Circuit = Gate  
Sequential Circuit = Gate + F/F

## ■ Flip-Flop


- ◆ The *storage elements* employed in clocked *sequential circuit*
- ◆ A binary cell capable of storing one bit of information

## ■ SR(*Set/Reset*) F/F

 

S	R	Q(t)	Q(t+1)
0	0	Q(t)	no change
0	1	0	clear to 0
1	0	1	set to 1
1	1	?	Indeterminate

## ■ D(*Data*) F/F

 


D	Q(t)	Q(t+1)
0	0	clear to 0
1	1	set to 1

- ◆ "no change" condition

- 1) Disable Clock
- 2) Feedback output into input


## ■ JK(*Jack/King*) F/F

 

J	K	Q(t)	Q(t+1)
0	0	Q(t)	no change
0	1	0	clear to 0
1	0	1	set to 1
1	1	Q(t)	Complement

- ◆ JK F/F is a refinement of the SR F/F
- ◆ The indeterminate condition of the SR type is defined in complement

## ■ T(*Toggle*) F/F

 


T	Q(t)	Q(t+1)
0	Q(t)	no change
1	Q'(t)	Complement


- ◆ T=1(J=K=1), T=0(J=K=0)

# FLIP FLOP


## ■ SR(*Set/Reset*) F/F

 


## ■ D(*Data*) F/F

 

## ■ JK(*Jack/King*) F/F

 


## ■ T(*Toggle*) F/F

 

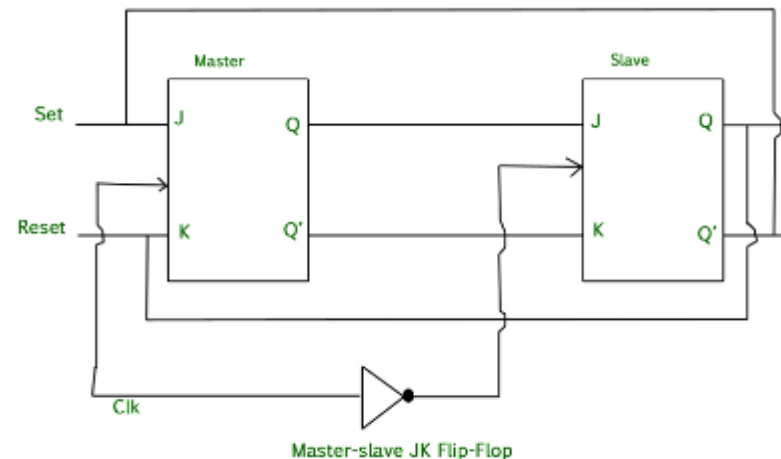
## Working of a master slave flip flop –

- When the clock pulse goes to 1, the slave is isolated; J and K inputs may affect the state of the system. The slave flip-flop is isolated until the CP goes to 0. When the CP goes back to 0, information is passed from the master flip-flop to the slave and output is obtained.
- Firstly the master flip flop is positive level triggered and the slave flip flop is negative level triggered, so the master responds before the slave.
- If  $J=0$  and  $K=1$ , the high  $Q'$  output of the master goes to the K input of the slave and the clock forces the slave to reset, thus the slave copies the master.
- If  $J=1$  and  $K=0$ , the high Q output of the master goes to the J input of the slave and the Negative transition of the clock sets the slave, copying the master.
- If  $J=1$  and  $K=1$ , it toggles on the positive transition of the clock and thus the slave toggles on the negative transition of the clock.
- If  $J=0$  and  $K=0$ , the flip flop is disabled and Q remains unchanged.


 
### Timing Diagram of a Master flip flop –



1. When the Clock pulse is high the output of master is high and remains high till the clock is low because the state is stored.
2. Now the output of master becomes low when the clock pulse becomes high again and remains low until the clock becomes high again.
3. Thus toggling takes place for a clock cycle.
4. When the clock pulse is high, the master is operational but not the slave thus the output of the slave remains low till the clock remains high.
5. When the clock is low, the slave becomes operational and remains high until the clock again becomes low.
6. Toggling takes place during the whole process since the output is changing once in a cycle.