


NOTE: Attempt ALL Questions Max Marks: 30 (Each Question carries 5 Marks)




Name:	Section:
Reg. No.:	Roll No.:
Date of Test:	

Believe you can and you are halfway there.


1. Find V_{AB} in the given network:

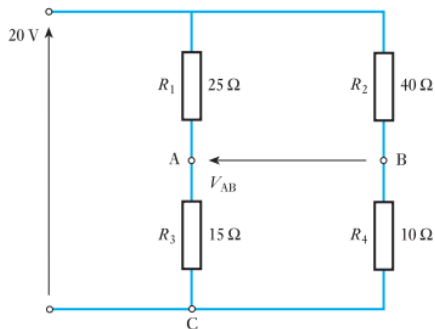

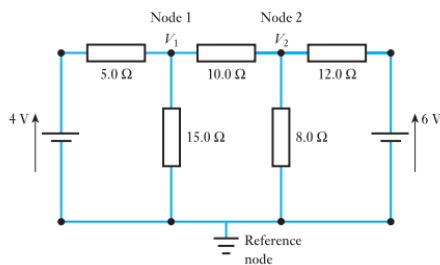
2. Find V_1 and V_2 in the circuit using **Nodal Analysis**. Also find the current across 8 ohm resistor:



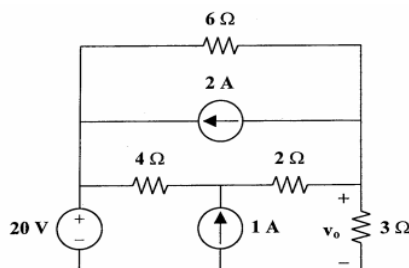3. Find v_0 using **Superposition** in the circuit:



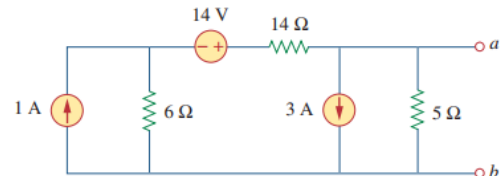4. Find **Norton equivalent** circuit across a and b terminals in the given circuit?



5. A series circuit with a resistor of 100Ω capacitor of $25\mu\text{F}$ and inductance of 0.15H is connected across 220-V, 60-Hz supply. Calculate (i) current (ii) power and (iii) power factor in the circuit.
6. Find i in the circuit when the source voltage $V_s = 50 \cos 200t$ volts.

