

Overview

- **Register Transfer Language**
- **Register Transfer**
- **Bus and Memory Transfers**
- **Logic Micro-operations**
- **Shift Micro-operations**
- **Arithmetic Logic Shift Unit**

Register Transfer Language

- **Combinational and sequential circuits can be used to create simple digital systems.**
- **These are the low-level building blocks of a digital computer.**
- **Simple digital systems are frequently characterized in terms of**
 - **the registers they contain, and**
 - **the operations that are performed on data stored in them**
- **The operations executed on the data in registers are called micro-operations e.g. shift, count, clear and load**

Register Transfer Language

Internal hardware organization of a digital computer :

- **Set of registers and their functions**
- **Sequence of microoperations performed on binary information stored in registers**
- **Control signals that initiate the sequence of micro-operations (to perform the functions)**

Register Transfer Language

- Rather than specifying a digital system in words, a specific notation is used, Register Transfer Language
- The symbolic notation used to describe the micro operation transfer among register is called a register transfer language
- For any function of the computer, the register transfer language can be used to describe the (sequence of) micro-operations
- Register transfer language
 - A symbolic language
 - A convenient tool for describing the internal organization of digital computers in concise/precise manner.
 - Can also be used to facilitate the design process of digital systems.

Register Transfer Language

- Registers are designated by capital letters, sometimes followed by numbers (e.g., A, R13, IR)
- Often the names indicate function:
 - MAR - memory address register
 - PC - program counter
 - IR - instruction register
- Registers and their contents can be viewed and represented in *various ways*
 - A register can be viewed as a single entity:




MAR

Register Transfer Language

- **Designation of a register**
 - a register
 - portion of a register
 - a bit of a register

 - **Common ways of drawing the block diagram of a register**



Register Transfer Language

- Copying the contents of one register to another is a register transfer
- A register transfer is indicated as

R2 ← R1

- In this case the contents of register R1 are copied (loaded) into register R2
- A simultaneous transfer of all bits from the source R1 to the destination register R2, during one clock pulse
- Note that this is a non-destructive; i.e. the contents of R1 are not altered by copying (loading) them to R2

Register Transfer Language

- A register transfer such as

$R3 \leftarrow R5$

Implies that the digital system has

- the data lines from the source register (R5) to the destination register (R3)
- Parallel load in the destination register (R3)
- Control lines to perform the action

Control Functions

- Often actions need to only occur if a certain condition is true
- This is similar to an “if” statement in a programming language
- In digital systems, this is often done via a *control signal*, called a control function
 - If the signal is 1, the action takes place
- This is represented as:

P: $R2 \leftarrow R1$


Which means “if $P = 1$, then load the contents of register R1 into register R2”, i.e., if ($P = 1$) then ($R2 \leftarrow R1$)

Hardware Implementation of Controlled Transfers


Implementation of controlled transfer

P: $R2 \leftarrow R1$

Block diagram

 

Timing diagram

 

- The same clock controls the circuits that generate the control function and the destination register
- Registers are assumed to use *positive-edge-triggered* flip-flops

Basic Symbols in Register Transfer

Symbols	Description	Examples
Capital letters	Denotes a register	MAR, R2
& Numerals Parentheses ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow \leftarrow	Denotes transfer of information	R2 \leftarrow R1
Colon :	Denotes termination of control function	P:
Comma ,	Separates two micro-operations	A \leftarrow B, B \leftarrow A

Overview


- Register Transfer Language
- Register Transfer
- **Bus and Memory Transfers**
- Logic Micro-operations
- Shift Micro-operations
- Arithmetic Logic Shift Unit

Connecting Registers - Bus Transfer

- In a digital system with many registers, it is impractical to have data and control lines to directly allow each register to be loaded with the contents of every possible other registers
- To completely connect n registers $\rightarrow n(n-1)$ lines
- $O(n^2)$ cost
 - This is not a realistic approach to use in a large digital system
- Instead, take a different approach
- Have one centralized set of circuits for data transfer – the bus
- **BUS STRUCTURE CONSISTS OF SET OF COMMON LINES, ONE FOR EACH BIT OF A REGISTER THROUGH WHICH BINARY INFORMATION IS TRANSFERRED ONE AT A TIME**
- Have control circuits to select which register is the source, and which is the destination

Connecting Registers - Bus Transfer

 
From a register to bus: $BUS \leftarrow R$



- One way of constructing common bus system is with **multiplexers**
- Multiplexer selects the source register whose binary information is kept on the bus.

- Construction of bus system for 4 register (Next Fig)
 - 4 bit register X 4
 - four 4X1 multiplexer
 - Bus selection S0, S1

Connecting Registers - Bus Transfer

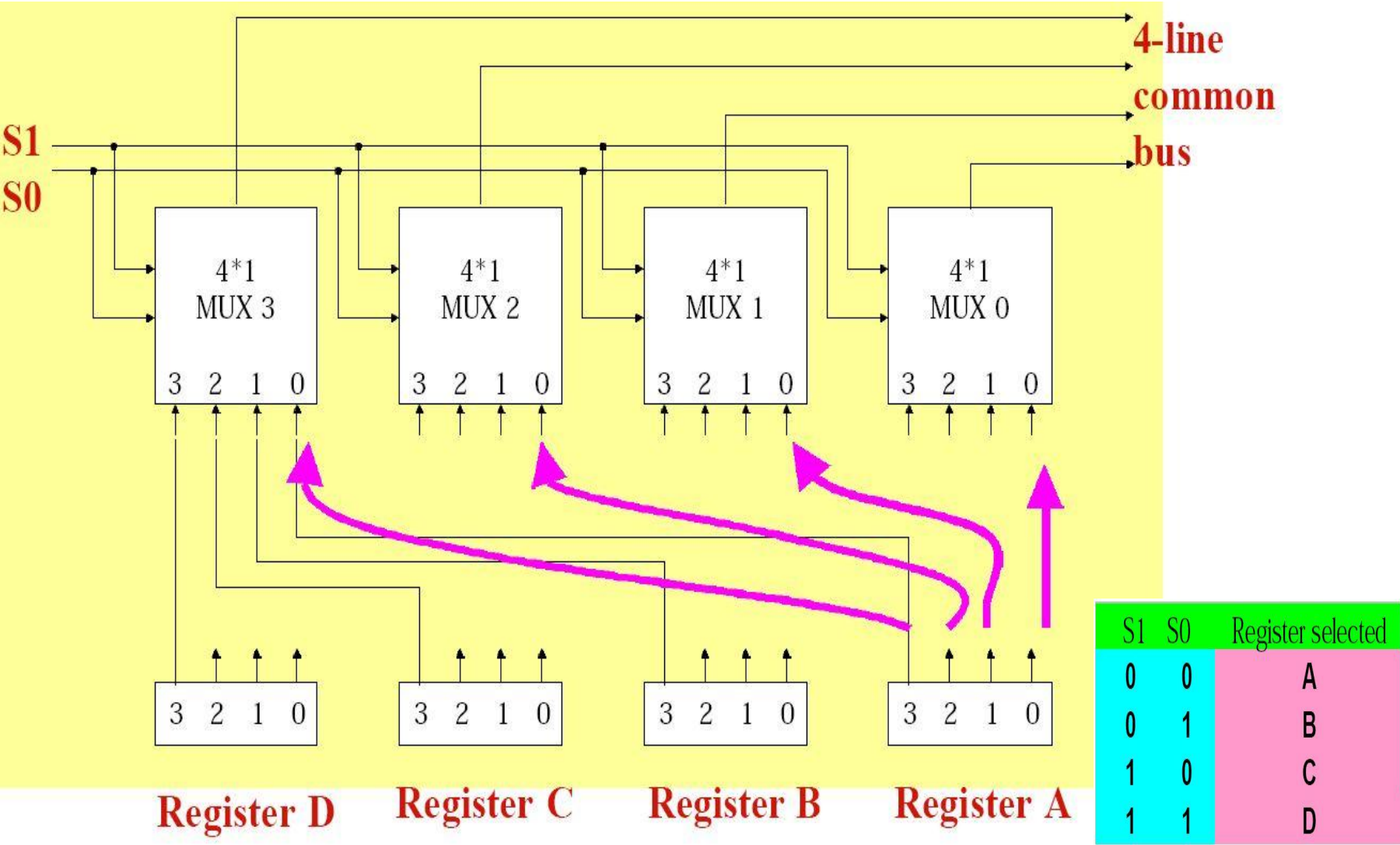


Connecting Registers - Bus Transfer

- For a bus system to multiplex **k registers** of **n bits** each
 - No. of multiplexer = n
 - Size of each multiplexer = k x 1

- **Construction of bus system for 8 register with 16 bits**
 - **16 bit register X 8**
 - **Sixteen 8X1 multiplexer**
 - **Bus selection S0, S1, S2**

Connecting Registers - Bus Transfer

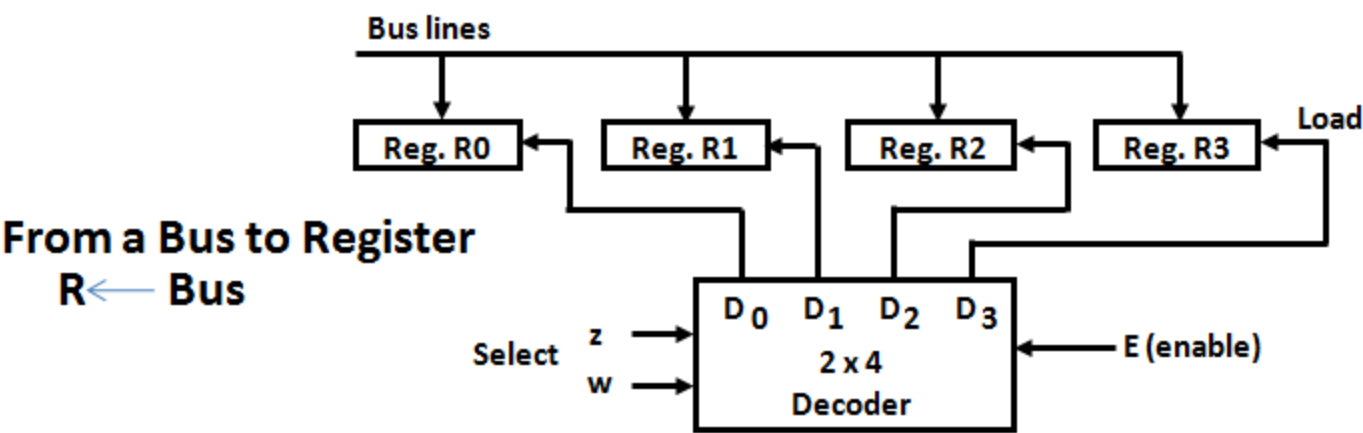


Connecting Registers - Bus Transfer

◆ Bus Transfer


- The content of register C is placed on the bus, and the content of the bus is loaded into register R1 by activating its load control input
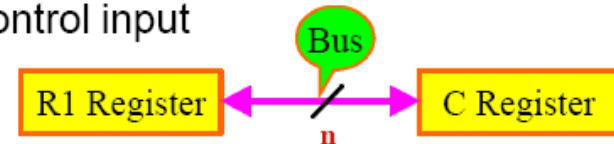
$$\left. \begin{array}{l} Bus \leftarrow C, R1 \leftarrow Bus \\ R1 \leftarrow C \end{array} \right\} =$$



◆ Three-State Bus Buffers


- A bus system can be constructed with **three-state gates** *instead of multiplexers*
- Tri-State : 0, 1, High-impedance(**Open circuit**)
- Buffer
 - » A device designed to be inserted between other devices to match impedance, to prevent mixed interactions, and **to supply additional drive or relay capability**
 - » Buffer types are classified as inverting or noninverting
- Tri-state buffer gate : Fig. 4-4
 - » When control input =1 : The output is enabled(output Y = input A)
 - » When control input =0 : The output is disabled(output Y = high-impedance)

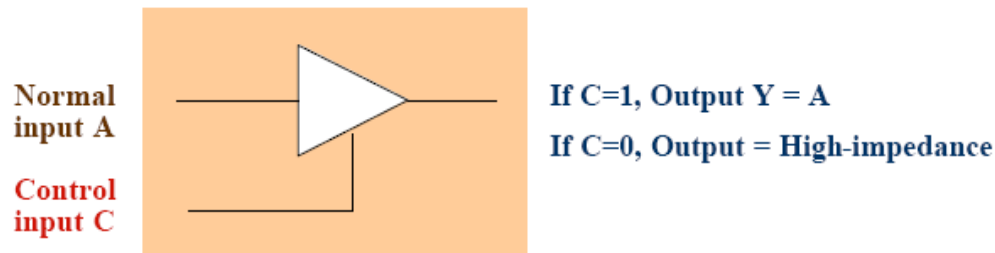

Connecting Registers - Bus Transfer

◆ The construction of a bus system with tri-state buffer : *Fig.*

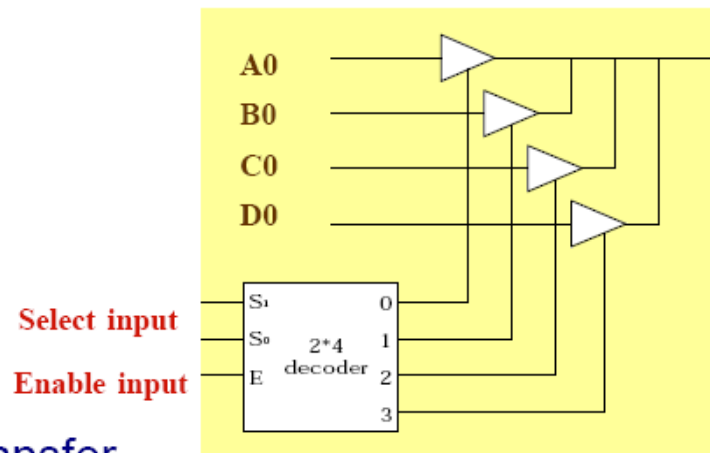- The outputs of four buffer are connected together to form a single bus line(Tri-state buffer)
- No more than one buffer may be in the active state at any given time(2 X 4 Decoder)
- To construct a common bus for 4 register with 4 bit : Fig.



AR: Address Reg.
DR: Data Reg.
M : Memory Word(Data)


READ : $DR \leftarrow M[AR]$
WRITE : $M[AR] \leftarrow R1$

◆ Memory Transfer

- Memory read : A transfer information into DR from the memory word M selected by the address in AR
- Memory Write : A transfer information from R1 into the memory word M selected by the address in AR


Memory - RAM

- Memory (RAM) can be thought as a sequential circuits containing some number of registers
- Memory stores binary information in groups of bits called **words**
- These registers hold the **words** of memory
- Each of the r registers is indicated by an *address*
- These addresses range from 0 to $r-1$
- Each register (word) can hold n bits of data
- Assume the RAM contains $r = 2^k$ words. It needs the following
 1. n data input lines
 2. n data output lines
 3. k address lines
 4. A Read control line
 5. A Write control line

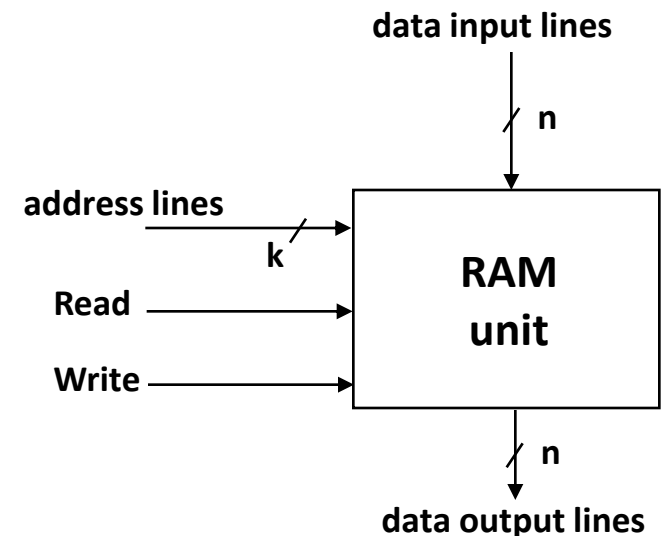

Memory Transfer

 Memory is usually accessed in computer systems by putting the desired address in a special register, the Memory Address Register (MAR, or AR)



Memory Read

- To read a value from a location in memory and load it into a register, the register transfer language notation looks like this:

$$R1 \leftarrow M[AR]$$

- This causes the following to occur
 1. The contents of the MAR get sent to the memory address lines
 2. A Read (= 1) gets sent to the memory unit
 3. The contents of the specified address are put on the memory's output data lines
 4. These get sent over the bus to be loaded into register R1

Memory Write

- To write a value from a register to a location in memory looks like this in register transfer language:

$$M[AR] \leftarrow R1$$

- This causes the following to occur
 1. The contents of the MAR get sent to the memory address lines
 2. A Write (= 1) gets sent to the memory unit
 3. The values in register R1 get sent over the bus to the data input lines of the memory
 4. The values get loaded into the specified address in the memory

SUMMARY OF R. TRANSFER MICROOPERATIONS

$A \leftarrow B$ $AR \leftarrow DR(AD)$ $A \leftarrow \text{constant}$ $ABUS \leftarrow R1, R2 \leftarrow ABUS$ AR DR M[R] M $DR \leftarrow M$ $M \leftarrow DR$	 1.Transfer content of reg. B into reg. A 2.Transfer content of AD portion of reg. DR into reg. AR 3.Transfer a binary constant into reg. A 4.Transfer content of R1 into bus A and, at the same time, transfer content of bus A into R2 5.Address register 6.Data register 7.Memory word specified by reg. R 8.Equivalent to M[AR] 9.Memory <i>read</i> operation: transfers content of memory word specified by AR into DR 10.Memory <i>write</i> operation: transfers content of DR into memory word specified by AR
---	---

MICROOPERATIONS

Computer system microoperations are of four types:

- **Register transfer microoperations**
- **Arithmetic microoperations**
- **Logic microoperations**
- **Shift microoperations**

Arithmetic MICROOPERATIONS

- The basic arithmetic microoperations are
 - Addition
 - Subtraction
 - Increment
 - Decrement
- The additional arithmetic microoperations are
 - Add with carry
 - Subtract with borrow
 - Transfer/Load
 - etc. ...

Summary of Typical Arithmetic Micro-Operations

$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow R2'$	Complement the contents of R2
$R2 \leftarrow R2' + 1$	2's complement the contents of R2 (negate)
$R3 \leftarrow R1 + R2' + 1$	subtraction
$R1 \leftarrow R1 + 1$	Increment
$R1 \leftarrow R1 - 1$	Decrement

Binary Adder

◆ 4-bit Binary Adder : *Fig. 4-6*

- Full adder = 2-bits sum + previous carry
- Binary adder = the arithmetic sum of two binary numbers of any length
- c_0 (input carry), c_4 (output carry)


 


Figure 4-6. 4-bit binary adder

Binary Adder-Subtractor

Binary Adder-Subtractor

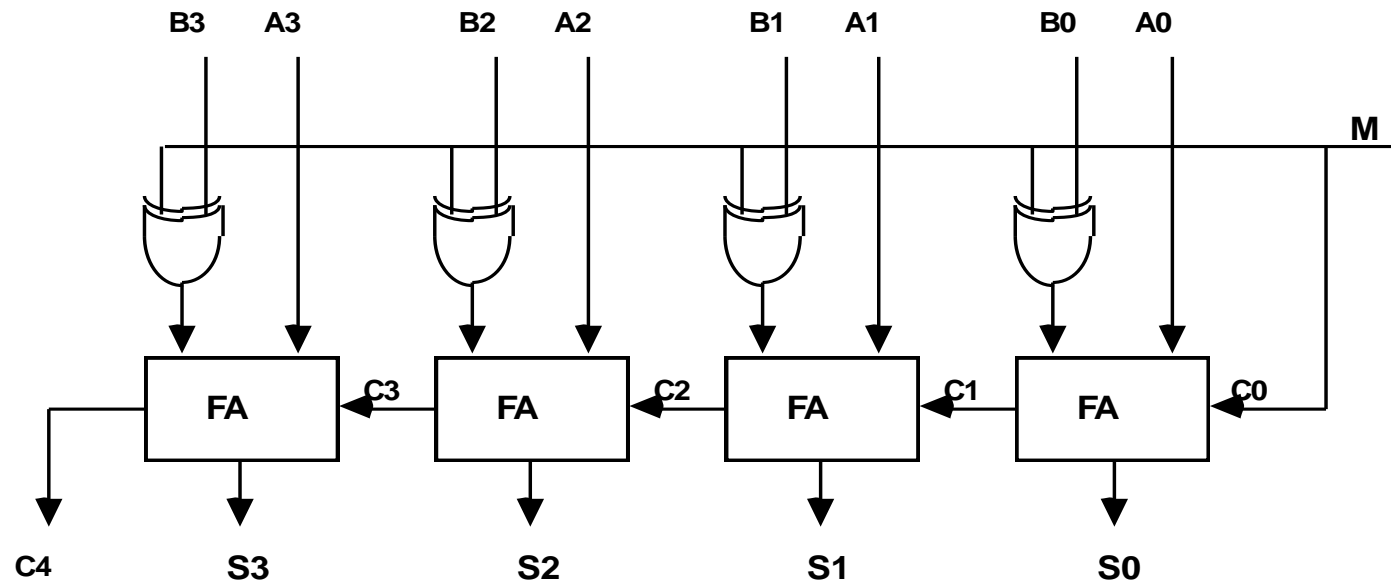


- Mode input M controls the operation
 - $M=0$ ---- adder
 - $M=1$ ---- subtractor

NOTE:

- $B \text{ xor } 0 = B$
- $B \text{ xor } 1 = B'$

Binary Incrementer


Binary Incrementer

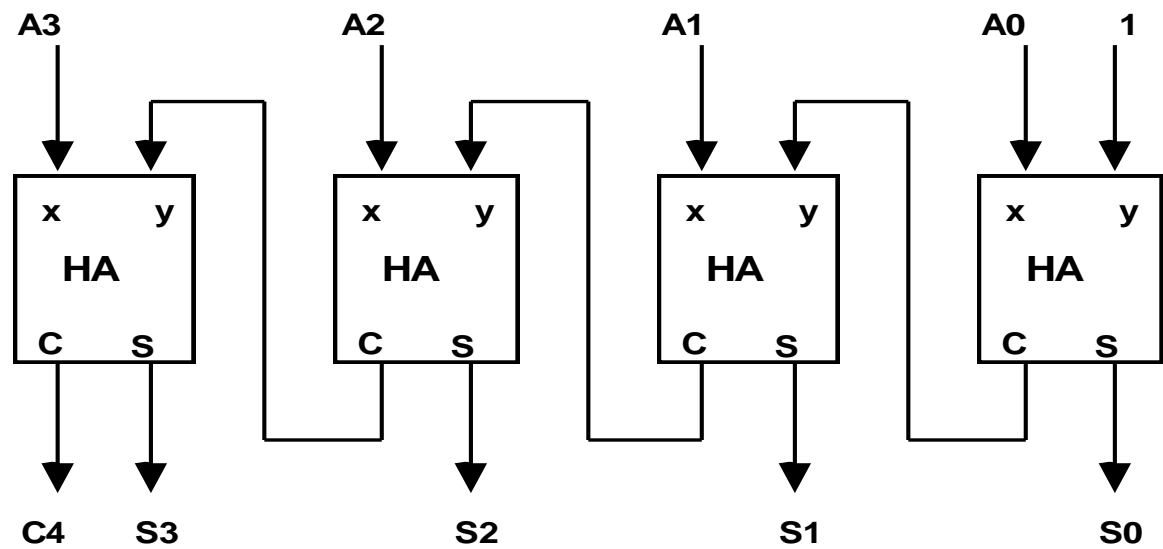

Assume example of 0110 as input
and Output must be 0111

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


(a) Truth table

 

(b) Logic diagram

Figure 1-16 Half-adder.

Arithmetic Circuits

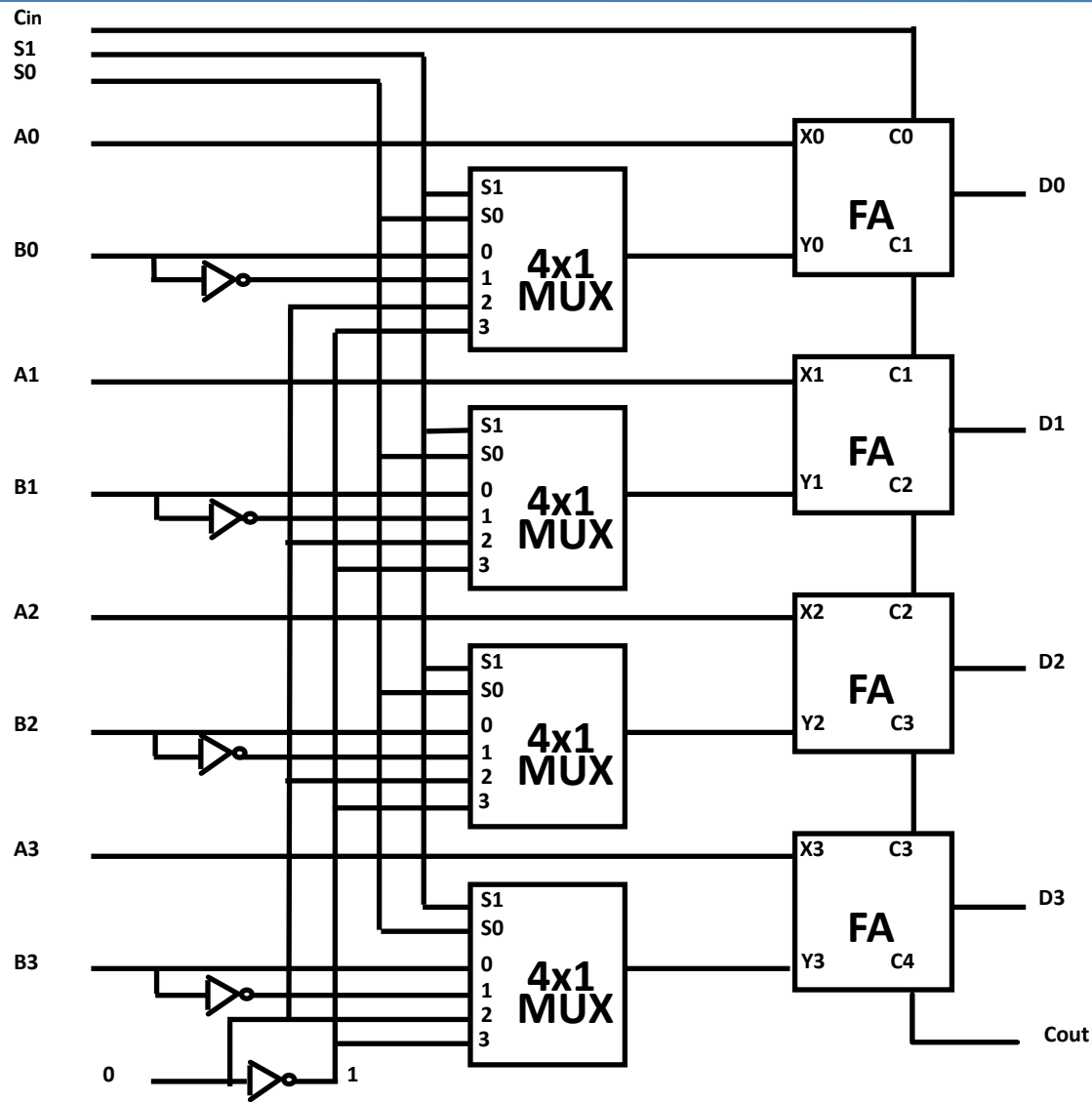

Select			Input	Output
S1	S0	C _{in}	Y	D=A+Y+C _{in}
0	0	0	B	D=A+B
0	0	1	B	D=A+B+1
0	1	0	B'	D=A+B'
0	1	1	B'	D=A+B'+1
1	0	0	0	D=A
1	0	1	0	D=A+1
1	1	0	1	D=A-1
1	1	1	1	D=A

Overview

- Register Transfer Language
- Register Transfer
- Bus and Memory Transfers
- Arithmetic Micro-operations
- **Logic Micro-operations**
- **Shift Micro-operations**
- **Arithmetic Logic Shift Unit**

Logic Micro operations

◆ Logic microoperation

- Logic microoperations consider *each bit of the register separately* and treat them as binary variables

» exam)

$$P: R1 \leftarrow R1 \oplus R2$$

$$\begin{array}{r} 1010 \text{ Content of R1} \\ + 1100 \text{ Content of R2} \\ \hline 0110 \text{ Content of R1 after P=1} \end{array}$$

- Special Symbols

» Special symbols will be adopted for the logic microoperations **OR**(\vee), **AND**(\wedge), and **complement**(*a bar on top*), to distinguish them from the corresponding symbols used to express Boolean functions

» exam)

$$P + Q: R1 \leftarrow R2 + R3, R4 \leftarrow R5 \vee R6$$

Logic OR

Arithmetic ADD

◆ List of Logic Microoperation

- Truth Table for 16 functions for 2 variables : **Tab. 4-5**
- 16 Logic Microoperation : **Tab. 4-6**

◆ Hardware Implementation

- 16 microoperation \rightarrow Use only 4(AND, OR, XOR, Complement)
- One stage of logic circuit

\therefore All other Operation can be derived

Logic Microoperations


X	Y	F ₀	F ₁	F ₂	F ₃	F ₄	F ₅	F ₆	F ₇	F ₈	F ₉	F ₁₀	F ₁₁	F ₁₂	F ₁₃	F ₁₄	F ₁₅
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

TABLE 4-5. Truth Table for 16 Functions of Two Variables

Boolean function	Microoperation	Name	Boolean function	Microoperation	Name
$F_0 = 0$	$F \leftarrow 0$	Clear	$F_8 = (x+y)'$	$F \leftarrow \overline{A \vee B}$	NOR
$F_1 = xy$	$F \leftarrow A \wedge B$	AND	$F_9 = (x \oplus y)'$	$F \leftarrow \overline{A \oplus B}$	Ex-NOR
$F_2 = xy'$	$F \leftarrow A \wedge \overline{B}$		$F_{10} = y'$	$F \leftarrow \overline{B}$	Compl-B
$F_3 = x$	$F \leftarrow A$	Transfer A	$F_{11} = x+y'$	$F \leftarrow A \vee \overline{B}$	
$F_4 = x'y$	$F \leftarrow \overline{A} \wedge B$		$F_{12} = x'$	$F \leftarrow \overline{A}$	Compl-A
$F_5 = y$	$F \leftarrow B$	Transfer B	$F_{13} = x'+y$	$F \leftarrow \overline{A} \vee B$	
$F_6 = x \oplus y$	$F \leftarrow A \oplus B$	Ex-OR	$F_{14} = (xy)'$	$F \leftarrow \overline{A \wedge B}$	NAND
$F_7 = x+y$	$F \leftarrow A \vee B$	OR	$F_{15} = 1$	$F \leftarrow \text{all 1's}$	set to all 1's

TABLE 4-6. Sixteen Logic Microoperations

Hardware Implementation

 

Function table

S_1	S_0	Output	μ -operation
0	0	$F = A \wedge B$	AND
0	1	$F = A \vee B$	OR
1	0	$F = A \oplus B$	XOR
1	1	$F = A'$	Complement

Applications of Logic Microoperations

- **Logic microoperations can be used to manipulate individual bits or a portions of a word in a register**
- **Consider the data in a register A. In another register, B, is bit data that will be used to modify the contents of A**
 - **Selective-set** $A \leftarrow A + B$
 - **Selective-complement** $A \leftarrow A \oplus B$
 - **Selective-clear** $A \leftarrow A \bullet B'$
 - **Mask (Delete)** $A \leftarrow A \bullet B$
 - **Clear** $A \leftarrow A \oplus B$
 - **Insert** $A \leftarrow (A \bullet B) + C$
 - **Compare** $A \leftarrow A \oplus B$

Applications of Logic Microoperations

1. In a selective set operation, the bit pattern in B is used to *set* certain bits in A

$$\begin{array}{ll} 1\ 1\ 0\ 0 & A_t \\ 1\ 0\ 1\ 0 & B \\ 1\ 1\ 1\ 0 & A_{t+1} \end{array} \quad (A \leftarrow A + B)$$

If a bit in B is set to 1, that same position in A gets set to 1, otherwise that bit in A keeps its previous value

2. In a selective complement operation, the bit pattern in B is used to *complement* certain bits in A

$$\begin{array}{ll} 1\ 1\ 0\ 0 & A_t \\ 1\ 0\ 1\ 0 & B \\ 0\ 1\ 1\ 0 & A_{t+1} \end{array} \quad (A \leftarrow A \oplus B)$$

If a bit in B is set to 1, that same position in A gets complemented from its original value, otherwise it is unchanged

Applications of Logic Microoperations

3. In a **selective clear** operation, the bit pattern in B is used to *clear* certain bits in A

1 1 0 0 A_t

1 0 1 0 B

0 1 0 0 A_{t+1} ($A \leftarrow A \cdot B'$)

If a bit in B is set to 1, that same position in A gets set to 0, otherwise it is unchanged

4. In a **mask** operation, the bit pattern in B is used to *clear* certain bits in A

1 1 0 0 A_t

1 0 1 0 B

1 0 0 0 A_{t+1} ($A \leftarrow A \cdot B$)

If a bit in B is set to 0, that same position in A gets set to 0, otherwise it is unchanged

Applications of Logic Microoperations

5. In a **clear** operation, if the bits in the same position in A and B are the same, they are cleared in A, otherwise they are set in A

1 1 0 0 A_t

1 0 1 0 B

0 1 1 0 A_{t+1} $(A \leftarrow A \oplus B)$

Applications of Logic Microoperations


6. An insert operation is used to introduce a specific bit pattern into A register, leaving the other bit positions unchanged

This is done as


- A mask operation to clear the desired bit positions, followed by
- An OR operation to introduce the new bits into the desired positions
- Example
 - Suppose you wanted to introduce 1010 into the low order four bits of A:
 - | | |
|---------------------|--------------|
| 1101 1000 1011 0001 | A (Original) |
| 1101 1000 1011 1010 | A (Desired) |
 - | | |
|---------------------|------------------|
| 1101 1000 1011 0001 | A (Original) |
| 1111 1111 1111 0000 | Mask |
| 1101 1000 1011 0000 | A (Intermediate) |
| 0000 0000 0000 1010 | Added bits |
| 1101 1000 1011 1010 | A (Desired) |

Shift Microoperations

 - There are three types of shifts
 - *Logical shift*
 - *Circular shift*
 - *Arithmetic shift*
- What differentiates them is the information that goes into the serial input
- A right shift operation




- A left shift operation

 


Logical Shift

 - In a logical shift the serial input to the shift is a 0.
- A right logical shift operation:




- A left logical shift operation:

 


- In a Register Transfer Language, the following notation is used
 - *shl* for a logical shift left
 - *shr* for a logical shift right
 - Examples:
 - $R2 \leftarrow shr\ R2$
 - $R3 \leftarrow shl\ R3$

Circular Shift

 - In a circular shift the serial input is the bit that is shifted out of the other end of the register.
- A right circular shift operation:




- A left circular shift operation:

 


- In a RTL, the following notation is used
 - *cil* for a circular shift left
 - *cir* for a circular shift right
 - Examples:
 - $R2 \leftarrow cir\ R2$
 - $R3 \leftarrow cil\ R3$

Arithmetic Shift

- An arithmetic shift is meant for signed binary numbers (integer)
- An arithmetic left shift **multiplies** a signed number **by two**
- An arithmetic right shift **divides** a signed number **by two**
- Sign bit : 0 for positive and 1 for negative
- The main distinction of an arithmetic shift is that it must keep the sign of the number the same as it performs the multiplication or division
- A right arithmetic shift operation:

 


- A left arithmetic shift operation:

 

Arithmetic Shift

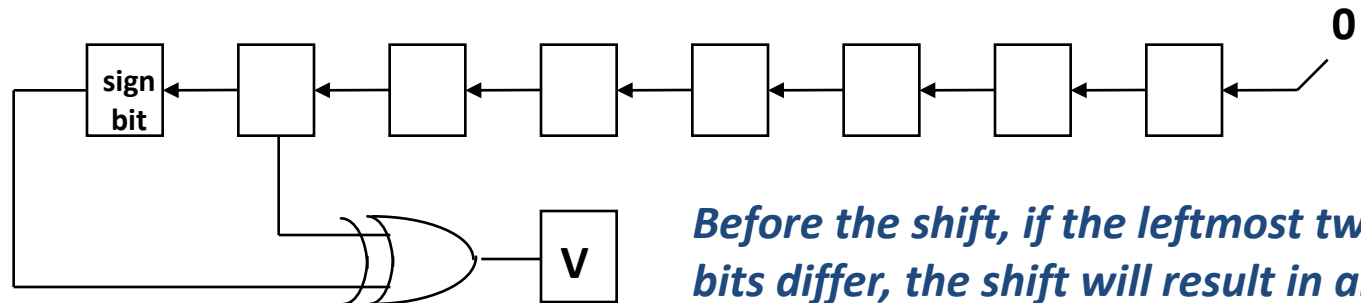- An left arithmetic shift operation must be checked for the overflow




Before the shift, if the leftmost two bits differ, the shift will result in an overflow

- In a RTL, the following notation is used
 - *ashl* for an arithmetic shift left
 - *ashr* for an arithmetic shift right
 - Examples:
 - » $R2 \leftarrow ashr R2$
 - » $R3 \leftarrow ashl R3$

Hardware Implementation of Shift Microoperation

◆ Hardware Implementation(Shifter) :

 

Function Table

Select	output			
	H0	H1	H2	H3
0	IR	A0	A1	A2
1	A1	A2	A3	IL

Arithmetic Logic and Shift Unit

