

ECE213: Digital Electronics




Ajmer Singh



9988921373



ajmer.17381@lpu.co.in

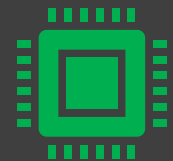

The Course Contents

Unit II

Combinational Logic System : Truth table, Basic logic operation, Boolean Algebra, Basic postulates, Standard representation of logic functions - SOP forms, Simplification of switching functions - K-map, Synthesis of combinational logic circuits, Logic gates, Fundamental theorems of Boolean algebra, Standard representation of logic functions POS forms

AB		00	01	11	10
CD	00	0	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	1	1	1

Combinational Logic System

★ Truth table It is set of all the possible inputs and outputs.

2-Variable

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	0

How many 2-Var Boolean function exist ^{max} $2^n = 16$
 when $n=2$

3-Variable

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

How many 3-Var fn. ^{max} $2^n = 2^3 = 2^8 = 256$

4-Variable

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

How many 4-Var fn ^{max} $2^n = 65536$

Combinational Logic System

★ Basic logic operation AND, OR, NOT

AND! Both or all the inputs need to be true for true o/p.

OR! Any one of the input need to be true for true o/p.

NOT! Input needs to be false for true o/p.

Combinational Logic System

Basic logic operation - Logic gates

- Basic Logic Gates (AND, OR, NOT)
- Universal Logic Gates (NAND, NOR)
- Derived Logic Gates (XOR, XNOR)

Gate	logic	Truth Table	Equation	Symbol															
AND	If <u>any</u> of the input is <u>low</u> the <u>o/p</u> is <u>low</u> , and if <u>all</u> the <u>inputs</u> are <u>high</u> the <u>o/p</u> is <u>high</u>	<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1	$Y = AB$	
A	B	Y																	
0	0	0																	
0	1	0																	
1	0	0																	
1	1	1																	
OR	If <u>any</u> of the <u>input</u> is <u>high</u> the <u>o/p</u> is <u>high</u> , and if <u>all</u> the <u>inputs</u> are <u>low</u> the <u>o/p</u> is <u>low</u>	<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	1	$Y = A + B$	
A	B	Y																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	1																	

Combinational Logic System

Basic logic operation - Logic gates


Gate logic

NAND

If any of the input is low the o/p is high. and if all the inputs are high the o/p is low.

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

$$Y = \overline{AB}$$

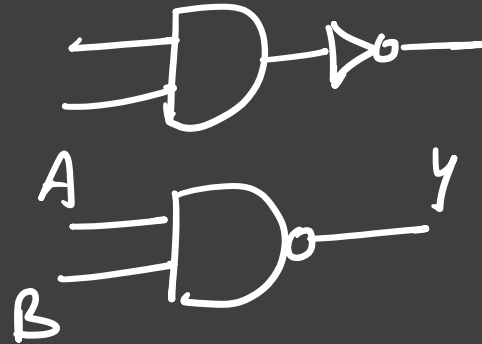


NOR

If any of the input is high the o/p is low, and if all the inputs are low the o/p is high.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

$$Y = \overline{A+B}$$


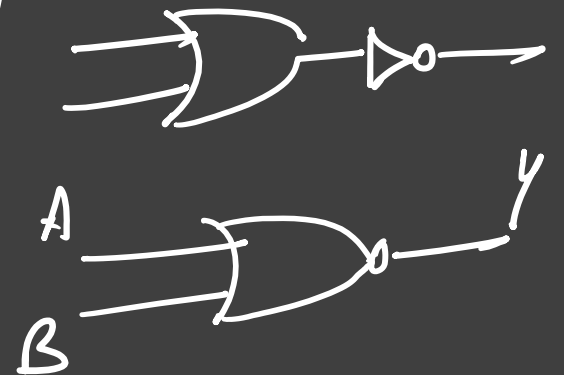


Combinational Logic System

Basic logic operation - Logic gates

Q! If any of the input is high the o/p is low.

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

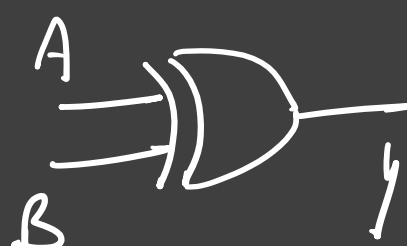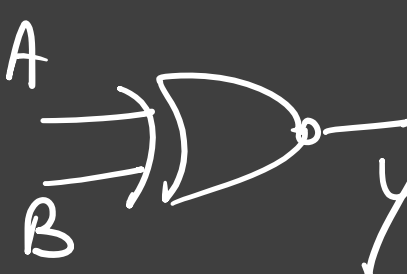Gate	logic																		
XOR	If both the inputs are same the o/p is low. otherwise the o/p is high	<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	0	$Y = A\bar{B} + \bar{A}B$ $Y = A \oplus B$ $Y = \overline{AB + \bar{A}\bar{B}}$ $Y = \overline{A \odot B}$	
A	B	Y																	
0	0	0																	
0	1	1																	
1	0	1																	
1	1	0																	
XNOR	If both the inputs are same the o/p is high, otherwise the o/p is low.	<table><tr><th>A</th><th>B</th><th>Y</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	Y	0	0	1	0	1	0	1	0	0	1	1	1	$Y = AB + \bar{A}\bar{B}$ $Y = A \odot B$ $Y = \overline{A\bar{B} + \bar{A}B}$ $Y = \overline{A \oplus B}$	
A	B	Y																	
0	0	1																	
0	1	0																	
1	0	0																	
1	1	1																	

Combinational Logic System

Boolean Algebra - Basic postulates

★ AND

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

★ Invert / NOT

$$\overline{0} = 1$$

$$\overline{1} = 0$$

★ OR

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

OR operator

Boolean

Binary Num's

$$1 + 1 = 10$$

Sum operator

Combinational Logic System

Boolean Algebra - Fundamental theorems of Boolean algebra

① Complementation law

$$\overline{0} = 1$$

$$\overline{1} = 0$$

$$\text{if } A = 0 \text{ then } \overline{A} = 1$$

$$\text{if } A = 1 \text{ then } \overline{A} = 0$$

$$\overline{\overline{A}} = A$$

② AND Law

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A = A$$

$$A \cdot \overline{A} = 0$$

③ OR Law

$$A + 0 = A$$

$$A + 1 = 1$$

$$A + A = A$$

$$A + \overline{A} = 1$$

④ Commutative law

$$A + B = B + A$$

$$AB = BA$$

⑤ Associative Law

$$(A + B) + C = A + (B + C)$$

$$(AB)C = A(BC)$$

Ex

$$A + 1 = 1$$
$$0 + 1 = 1$$
$$1 + 1 = 1$$

Combinational Logic System

Boolean Algebra - Fundamental theorems of Boolean algebra

⑥ Distributive Law

$$A.(B+C) = AB+AC$$

$$A + BC = (A+B)(A+C)$$

⑦ Absorption Law

$$A + AB = A$$

$$\begin{aligned} & A + AB \\ \Rightarrow & A(1+B) \\ & = A \cdot 1 \\ & = A \end{aligned}$$

Combinational Logic System

Boolean Algebra - Fundamental theorems of Boolean algebra

⑧ De Morgan's Th.

$$\overline{AB} = \bar{A} + \bar{B}$$

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

Break the line,
change the sign

⑨ Duality

- Change all '+' to '.'
- Change all '.' to '+'
- Complement all '0' and '1'
- Don't complement the variable.

Ex

$$A \cdot \bar{A} = 0$$

Duality
 \Rightarrow

$$\underline{A + \bar{A} = 1}$$

Combinational Logic System

Boolean Algebra - Fundamental theorems of Boolean algebra

Ex Reduce the Boolean exp.

$$\begin{aligned} Y &= A + B(AC + (B + \bar{C})D) \\ &= A + BAC + B(B + \bar{C})D \\ &= A + BAC + BB D + B\bar{C}D \\ &= A + ABC + BD + B\bar{C}D \\ &= A(\underline{1 + BC}) + BD(\underline{1 + \bar{C}}) \end{aligned}$$

$$\boxed{Y = A + BD}$$