

# ECE213: Digital Electronics




Ajmer Singh



9988921373



ajmer.17381@lpu.co.in

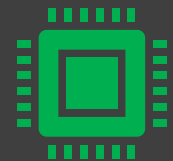



# The Course Contents

## Unit II

Combinational Logic System : Truth table, Basic logic operation, Boolean Algebra, Basic postulates, Standard representation of logic functions - SOP forms, Simplification of switching functions - K-map, Synthesis of combinational logic circuits, Logic gates, Fundamental theorems of Boolean algebra, Standard representation of logic functions POS forms

AB		00	01	11	10
CD	00	0	0	1	1
	01	0	0	1	1
	11	0	0	0	1
	10	0	1	1	1




# The Course Contents
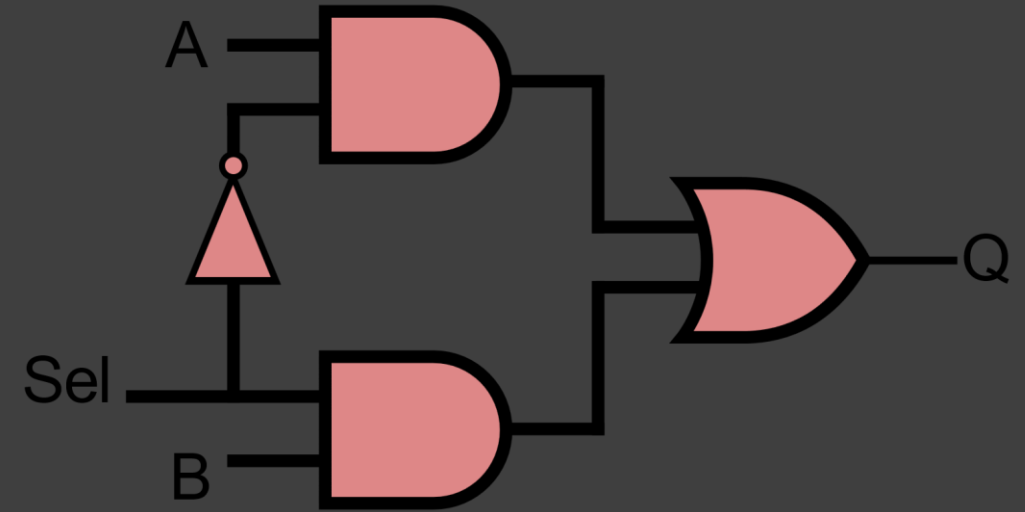
## Unit III

*Introduction to Combinational Logic Circuits : Adders, Subtractors, Comparators, Multiplexers and Demultiplexers, Decoders, Encoders, Parity circuits*

*Introduction to Logic Families : Introduction to different logic families, Structure and operations of TTL, MOS and CMOS logic families*



# Combinational Logic System

Simplification of switching functions - Karnaugh-map To reduce the Boolean function

★ For one variable function

A	$y_1$	$y_2$	$y_3$	$y_4$
0	0	1	0	1
1	1	0	0	1

$$y_1 = A$$

$$y_2 = \bar{A}$$

$$y_3 = 0$$

$$y_4 = 1$$

★ For two variable function

		LSB	
A	B	0	1
	0	0 0 1 0	0 1 1 0
1	1	1 0 1 1	1 1 1 1
		2	3

A	B	y
0	0	0
1	0	1
2	1	0
3	1	1

Q. How many no of cell we have in n-variables k-map

- A. (a)  $n$   
 (b)  $n+1$   
 (c)  $n^2$   
 (d)  $n \times n$
- all are wrong

$$2^n$$


$n=1$	2
$n=2$	4
$n=3$	8
$n=4$	16

# Combinational Logic System

## Simplification of switching functions - K-map


# Kmap reduce the function based on Grouping of Cells
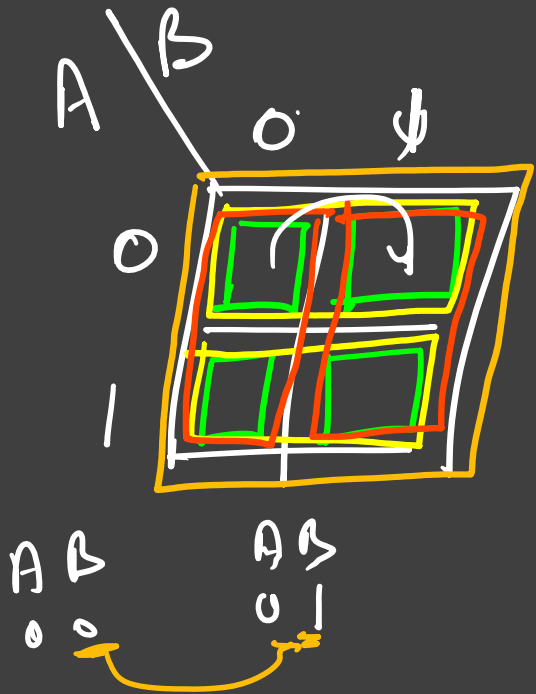
# Valid Grouping: When we move from one cell to another cell in the group, only one bit changes



★ Size of Group

$2^n$  , 1, 2, 4, 8, 16, 32, --

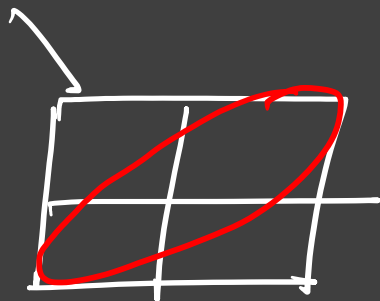

✗ No diagonal grouping is allowed

# Combinational Logic System

Simplification of switching functions - K-map

Ex: And logic

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

A \ B	0	1
0	0	0
1	0	1

for SOP — Make the Group of ones

A \ B	0	1
0	0	0
1	0	1

$$Y = AB$$

for POS — Make the Group of zeros

A \ B	0	1
0	0	0
1	0	1

$$Y = (A)(B) = AB$$

Note: Always make the largest possible groups

# Combinational Logic System

Simplification of switching functions - K-map

Ex OR Logic

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

For SOP

A \ B	0	1
0	0	1
1	1	1

$Y = A + B$

For POS

A \ B	0	1
0	0	1
1	1	1

$Y = (A + B)$

# Combinational Logic System

Simplification of switching functions - K-map

Ex XOR Gate

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

For SOP

A \ B	0	1
0	0	1
1	1	0

For POS

A \ B	0	1
0	0	1
1	1	0

$$Y = \bar{A}B + A\bar{B}$$

$$Y = (A+B) \cdot (\bar{A}+\bar{B})$$



# Combinational Logic System

## Simplification of switching functions - K-map

ex NAND Lox

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

for sol

A \ B	0	1
0	1	1
1	1	0

$$Y = \overline{A} + \overline{B}$$

$$Y = \overline{AB}$$

for pos

A \ B	0	1
0	1	1
1	1	0

$$Y = \overline{A} + \overline{B}$$