

ECE213: Digital Electronics




Ajmer Singh



9988921373



ajmer.17381@lpu.co.in

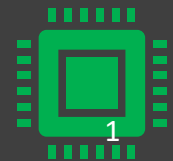



The Course Contents

Unit V

*Sequential Logic Circuits Applications : Registers:
Operation of all basic Shift Registers, Counters:
Design of Asynchronous and Synchronous counters,
Ring counter and Johnson ring counter*






Sequential Logic Circuits Applications

Johnson Ring Counter 4-bit
Twisted

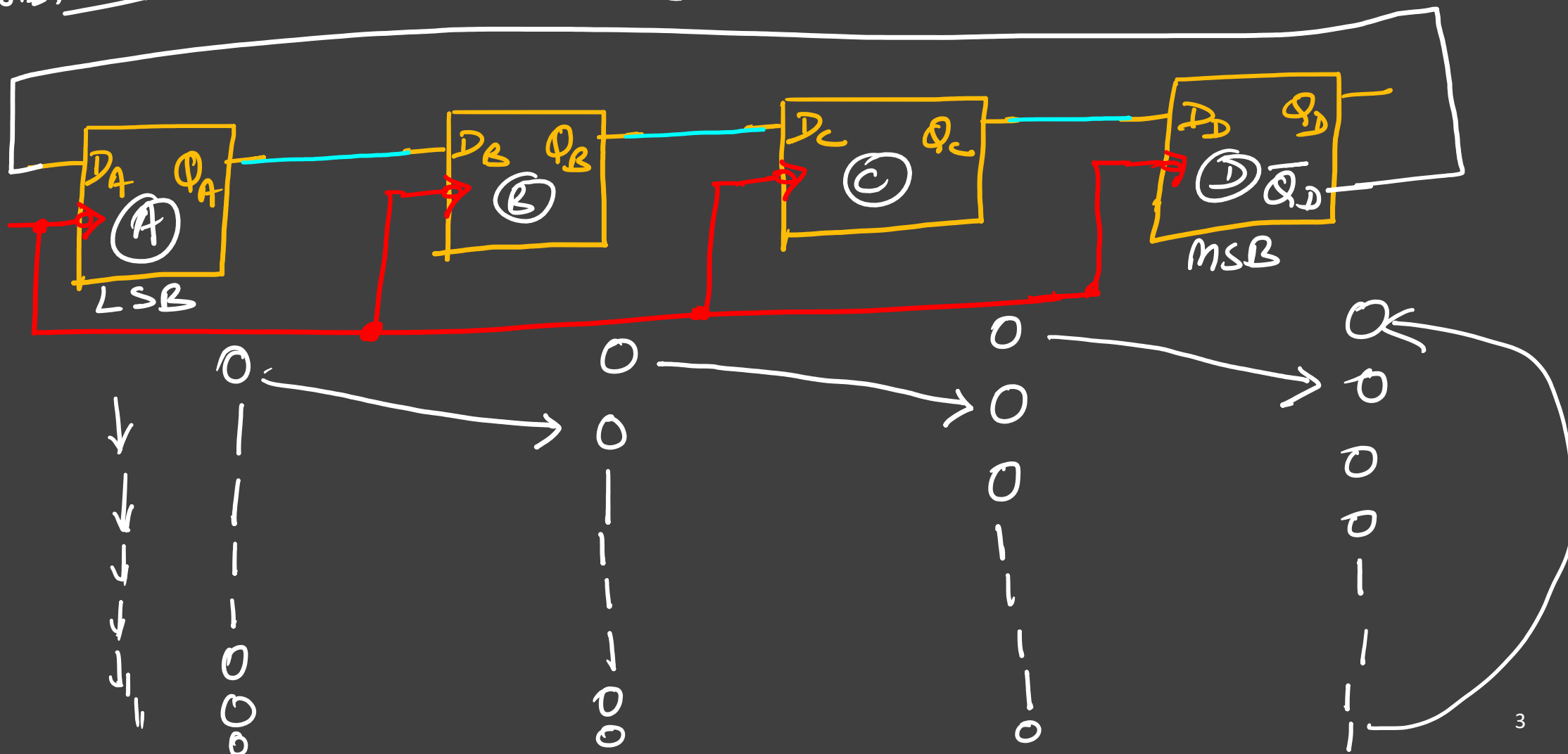
(MOD 8 Johnson Ring Counter)
(MOD $2n$ Johnson Counter)





Sequential Logic Circuits Applications

Johnson Ring Counter

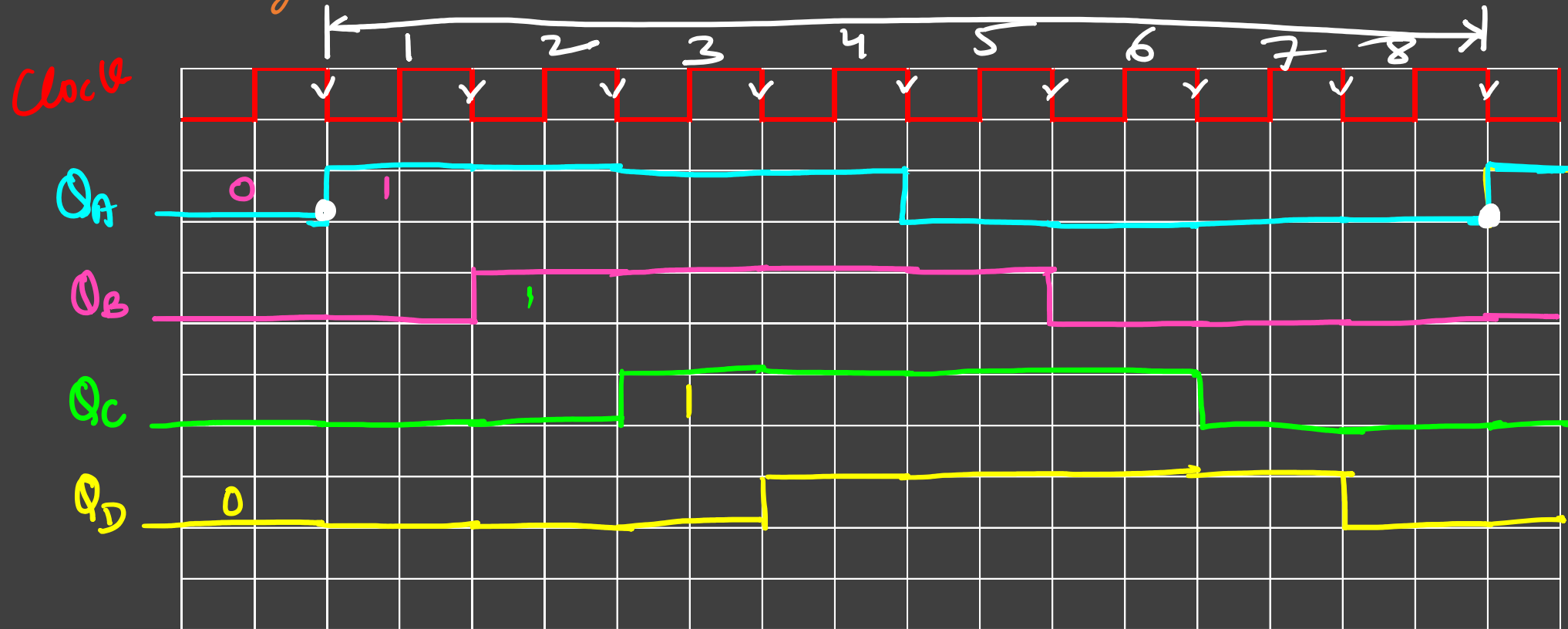

Sequential Logic Circuits Applications


Consider the following circuit involving three D-type flip-flops used in a certain type of counter configuration.

If at some instance prior to the occurrence of the clock edge, P, Q and R have a value 0, 1 and 0 respectively, what shall be the value of PQR after the clock edge?

→ +ve edge



- a) 000
- b) 001
- c) 010
- ☒ d) 011

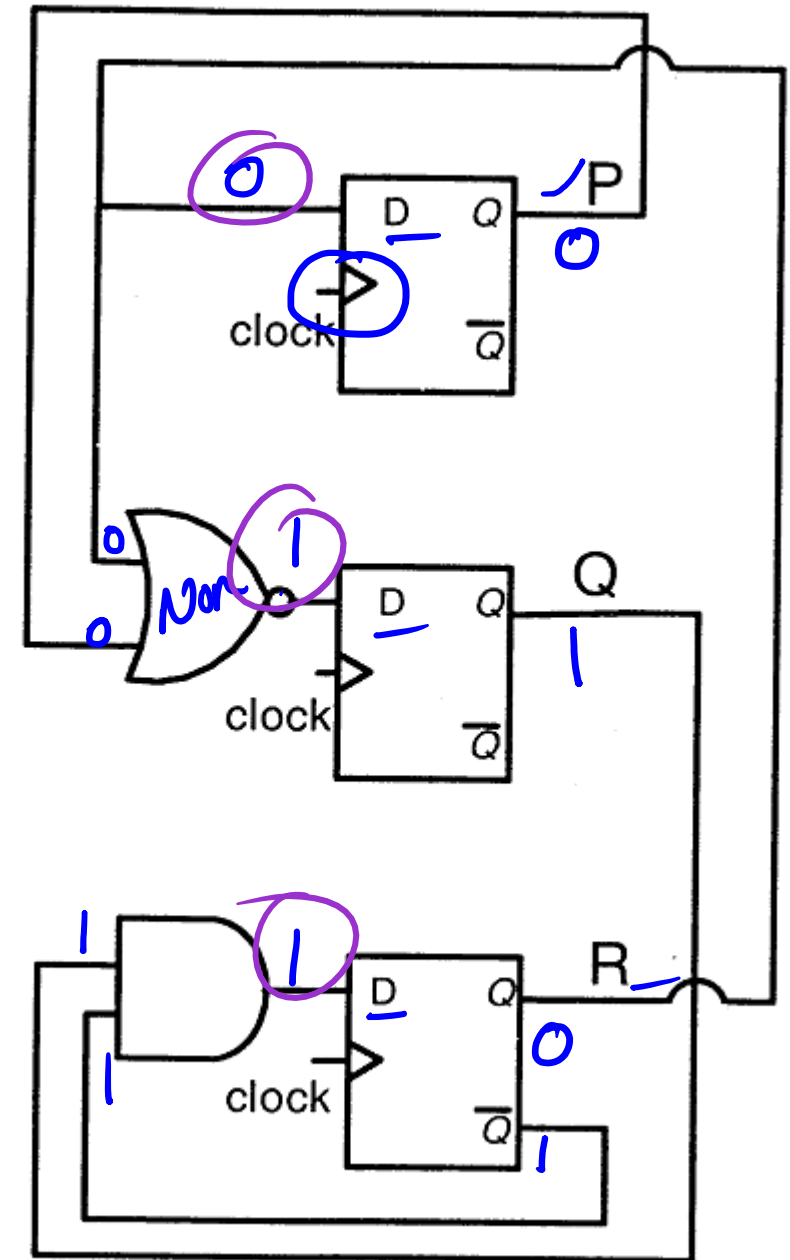

Sequential Logic Circuits Applications


In the sequential circuit shown below, if the initial value of the output Q_1Q_0 is 00, what are the next four values of Q_1Q_0 ?

- a) 11, 10, 01, 00
- b) 10, 11, 01, 00
- c) 10, 00, 01, 11
- d) 11, 10, 00, 01

00
11
10
01
01

0
3
2
1
0

2-bit
Down
Down

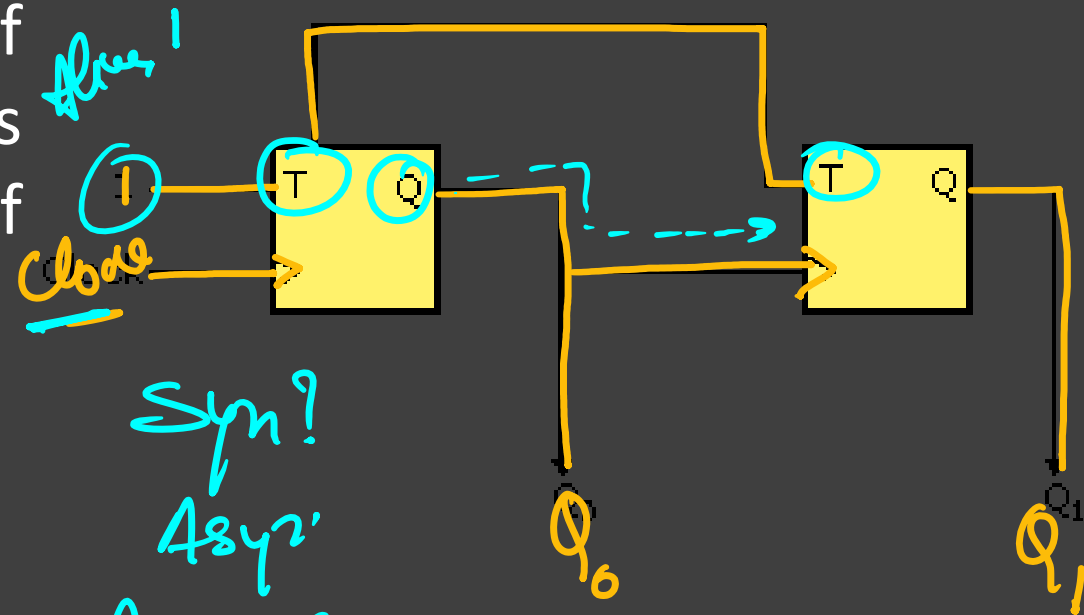

Syn?
Asyn?
Asyn Count

+ve edge
-ve edge

Q is for next FFs
Q

Sequential Logic Circuits Applications

Let $k = 2^n$. A circuit is built by giving the output of an n -bit binary counter as input to an n -to- 2^n bit decoder. This circuit is equivalent to a

- a) k -bit binary up counter.
- b) k -bit binary down counter.
- c) k -bit ring counter.
- d) k -bit Johnson counter

