

### Pre Lab Worksheet (Exp 3)

**Question 1:** Kindly apply the Thevenin or Norton theorem to find the value of current across 4 Ohm, if the input applied voltage is the last two digits of your roll number. (Example: for the Roll number: REX124A16 Input supply is 16 V)

