

ECE213: Digital Electronics




Ajmer Singh



9988921373



ajmer.17381@lpu.co.in

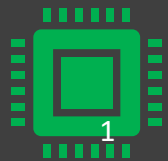



The Course Contents

Unit V



Sequential Logic Circuits Applications : Registers:
Operation of all basic Shift Registers, Counters:
Design of Asynchronous and Synchronous counters,
Ring counter and Johnson ring counter



Sequential Logic Circuits Applications ^{MSB} ^{LSB}

Registers 2-bit register!

$D = 10$

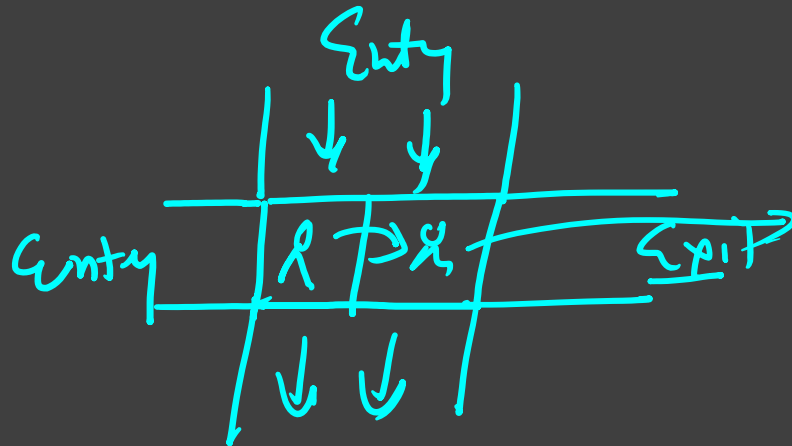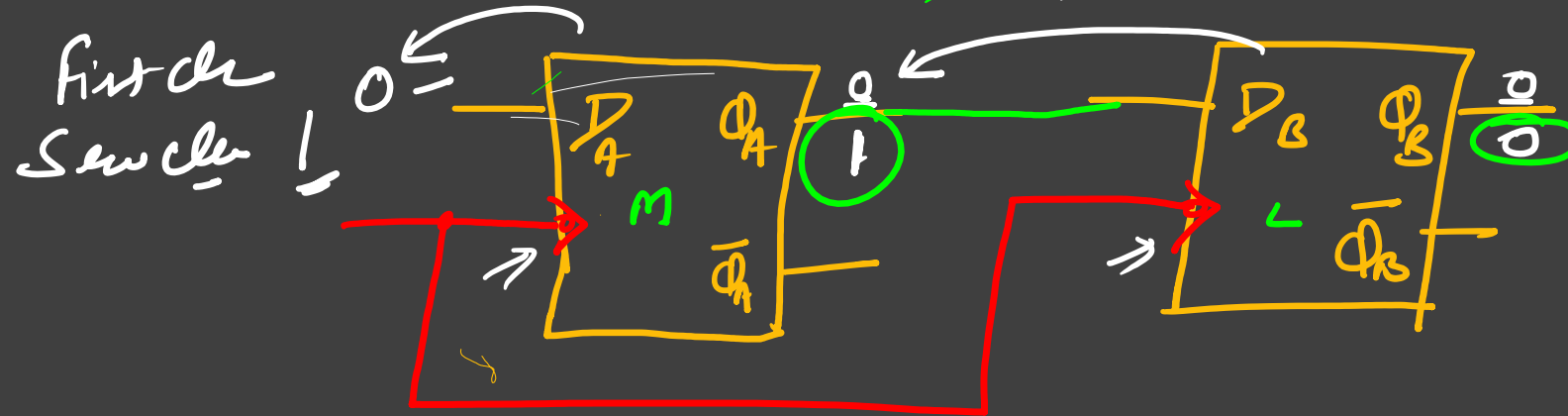

o/p
Serial
Parallel

o/p
Serial
Parallel

Sequential Logic Circuits Applications

Registers Shift registers

- 1) SISO (Serial in Serial out)
- 2) SIPO (Serial in Parallel out)
- 3) PISO (Parallel in Parallel out)
- 4) PISO (Parallel in Serial out)


Q: What is the need of shift register

- A:
- To shift the data
 - To store the data
 - To produce delay
 - To convert s/p
Serial or Parallel


Sequential Logic Circuits Applications

Registers 4-bit SISO

$D = 1101$

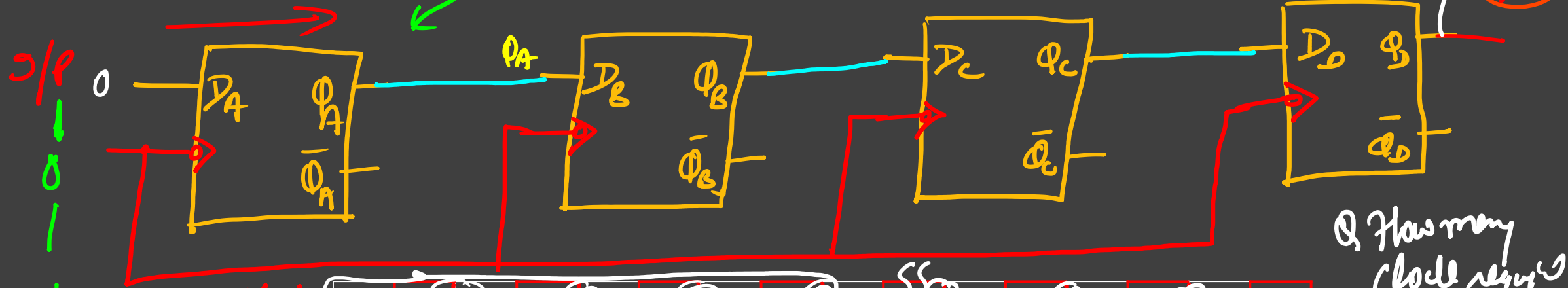

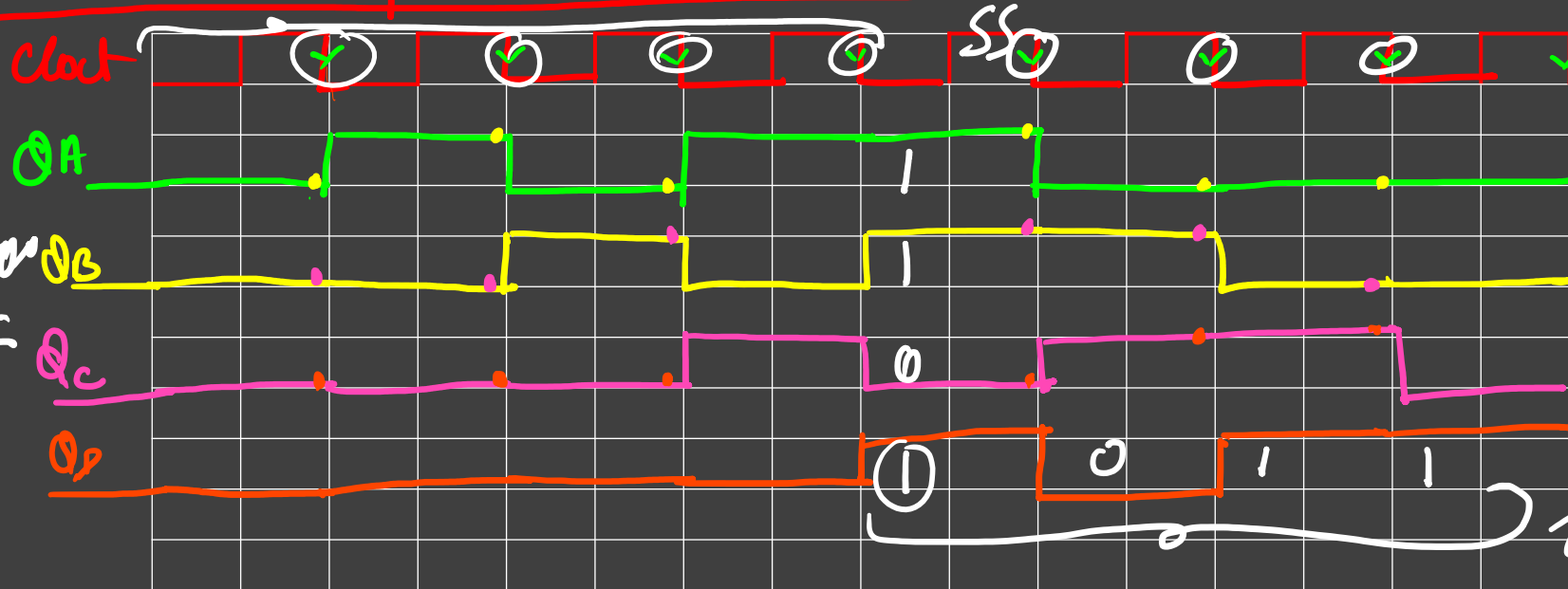Q How many total no. of clock require to store n bit data in serial mode
A: n clocks




Q How many clock require to read n bit data in serial mode
A: $n-1$

Lower 5


Sequential Logic Circuits Applications

Registers 4-bit SISO

$D = 1101$

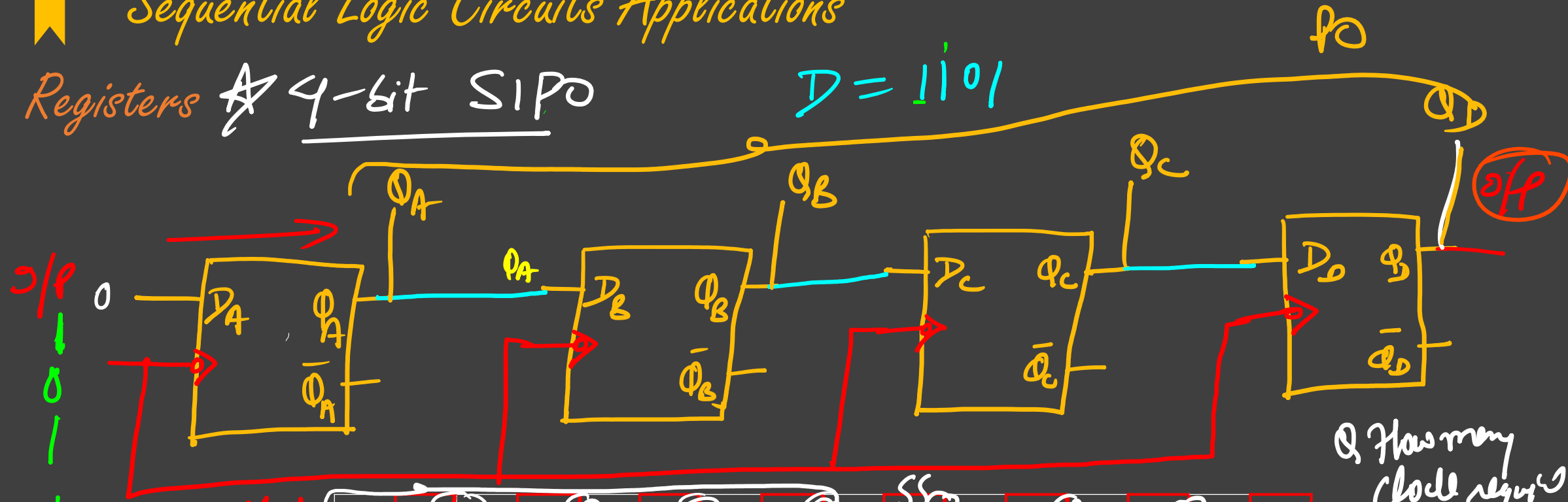

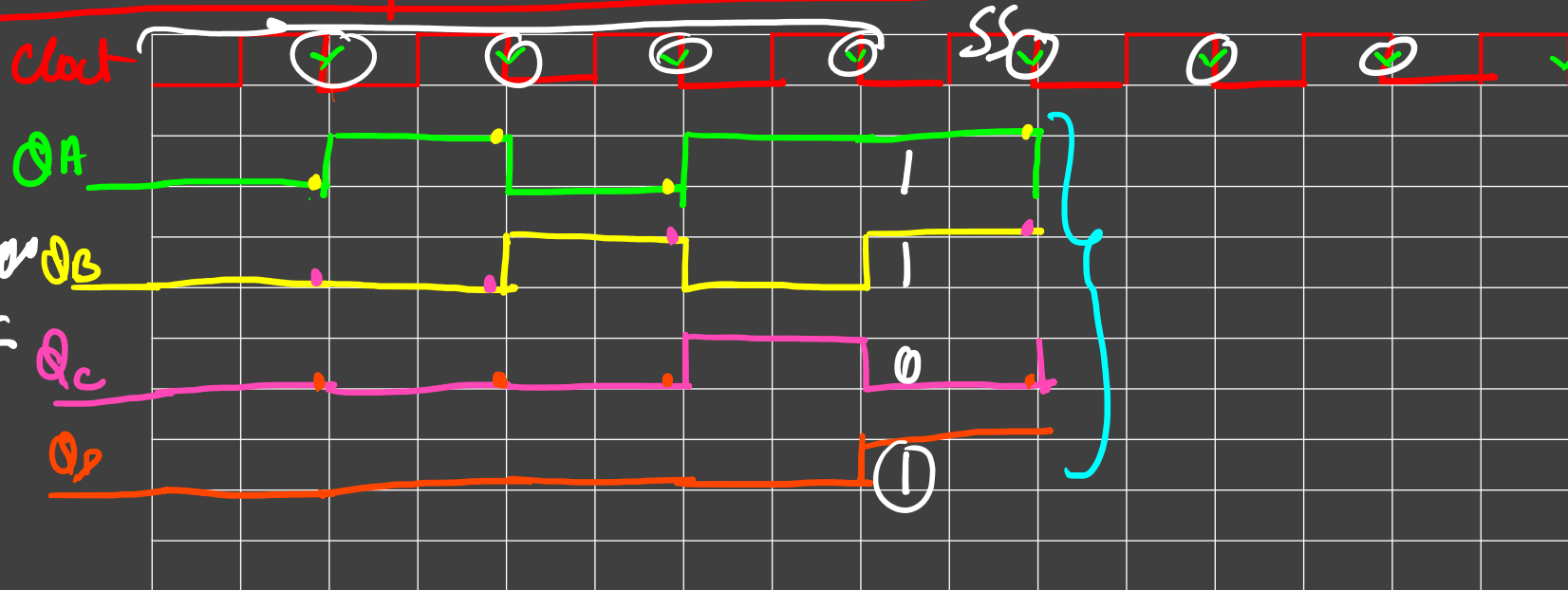Q How many total no. of clock require to store n bit data in serial mode
A: n clock




Q How many clock require to read n bit data in parallel mode
A: 2nd clock
No clock

Sequential Logic Circuits Applications

Registers ~~A~~ P/O shift reg.

parallel in

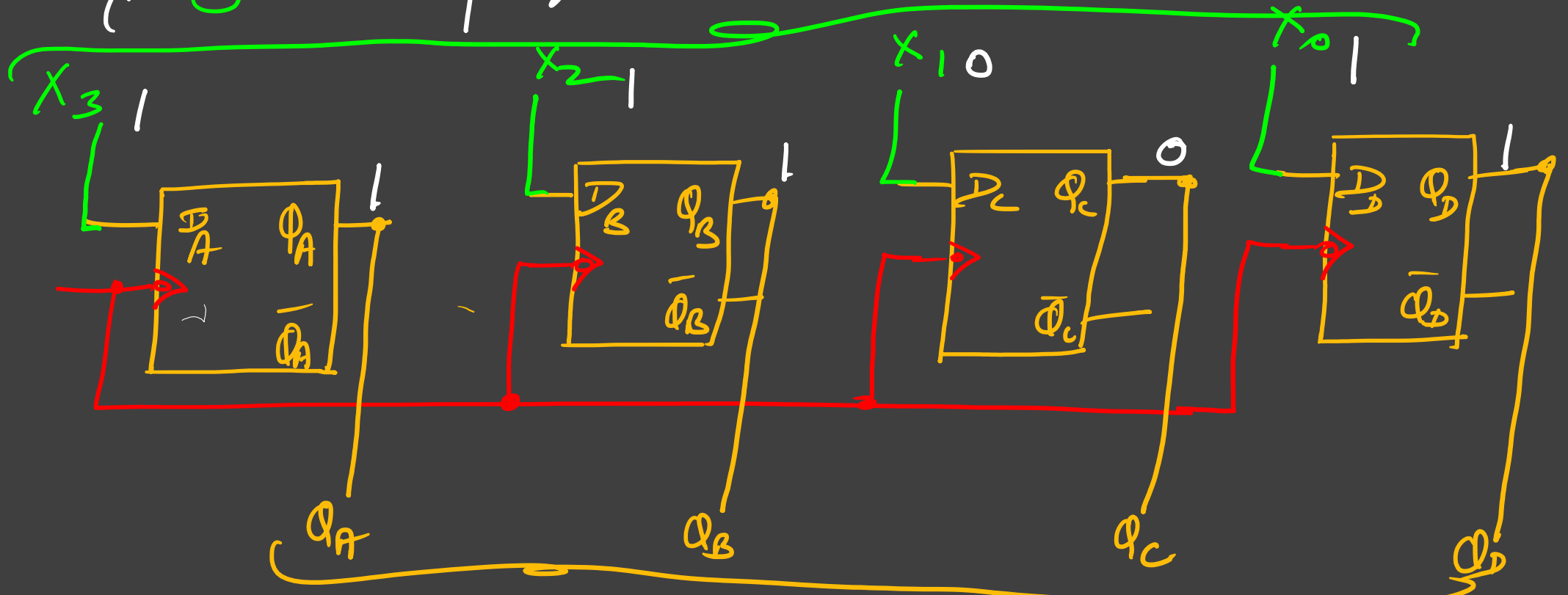

Q: How many clock pulses are required to write the 4-bit data parallel in and parallel out?

A: One clock pulse.