

ECE213: Digital Electronics




Ajmer Singh



9988921373



ajmer.17381@lpu.co.in

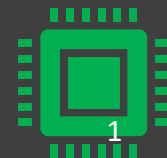



The Course Contents

Unit V

*Sequential Logic Circuits Applications : Registers:
Operation of all basic Shift Registers, Counters:
Design of Asynchronous and Synchronous counters,
Ring counter and Johnson ring counter*



Sequential Logic Circuits Applications

Registers Shift registers

- 1) SISO (Serial in Serial out)
- 2) SIPO (Serial in Parallel out)
- 3) PISO (Parallel in Parallel out)
- 4) PISO (Parallel in Serial out)


Q: What is the need of shift register

- A:
- To shift the data
 - To store the data
 - To produce delay
 - To convert s/p
Serial or Parallel


Sequential Logic Circuits Applications

Registers 4-bit SISO

$D = 1101$

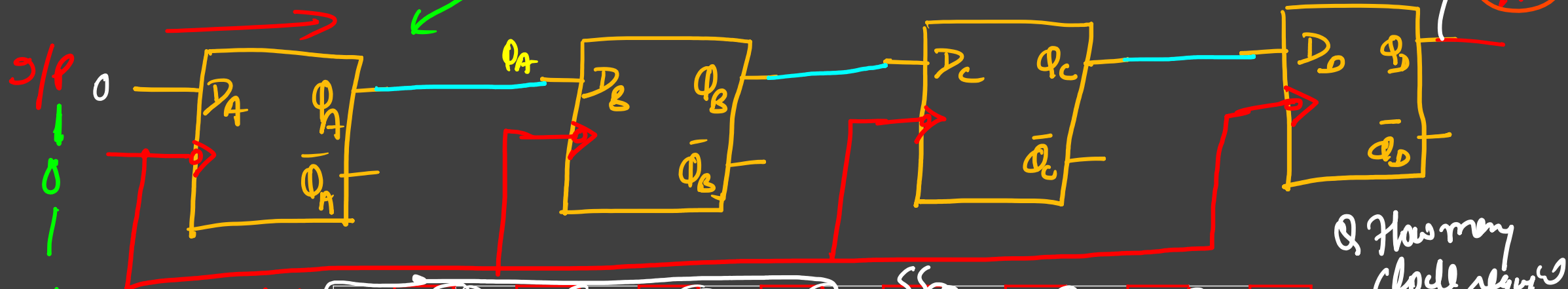

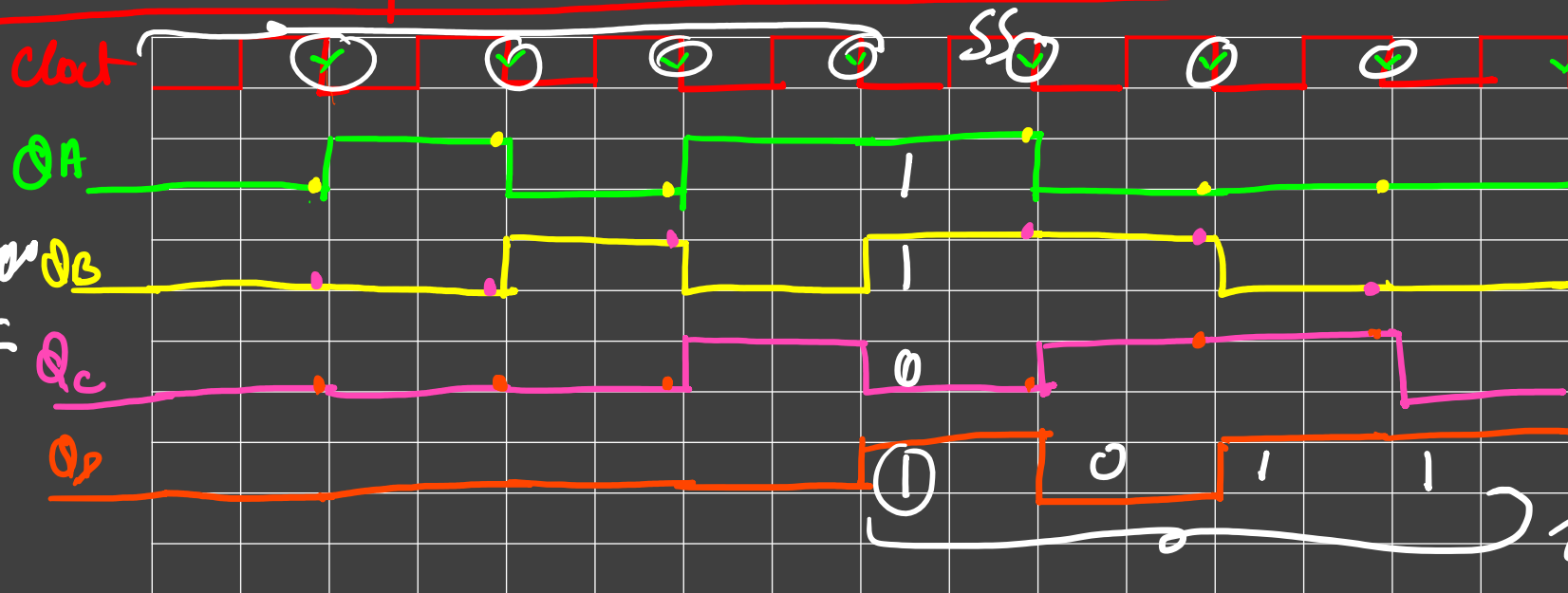Q How many total no. of clock require to store n bit data in serial mode
A: n clocks




Q How many clock require to read n bit data in serial mode
A: $n-1$

Lower 4


Sequential Logic Circuits Applications

Registers 4-bit SISO

$D = 1101$

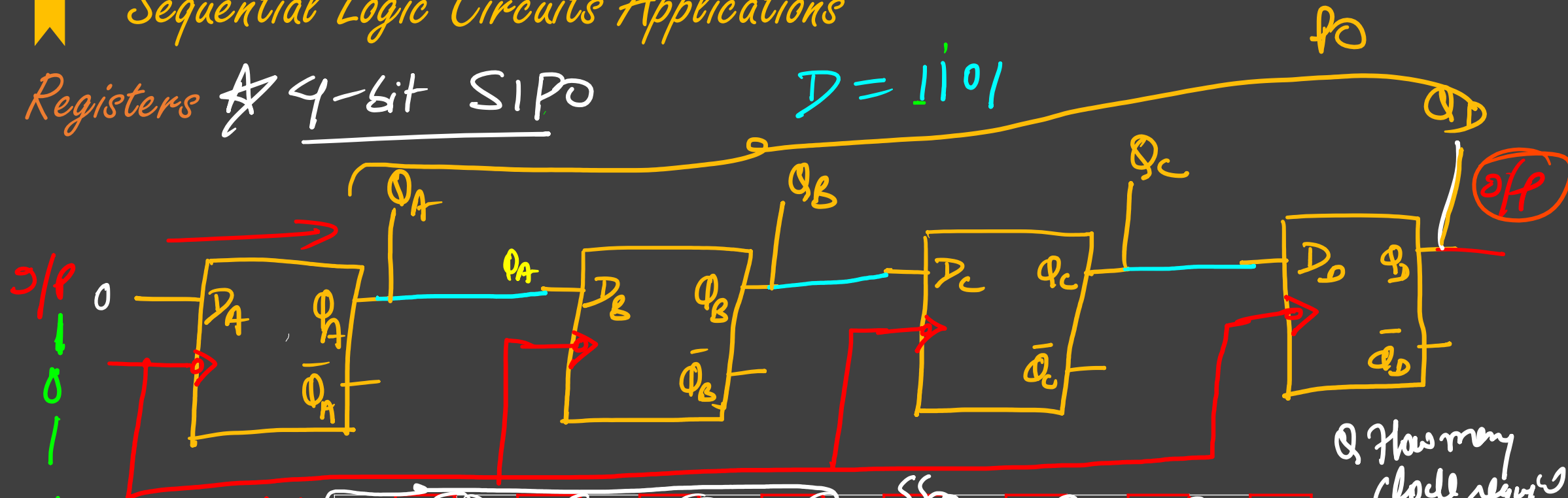

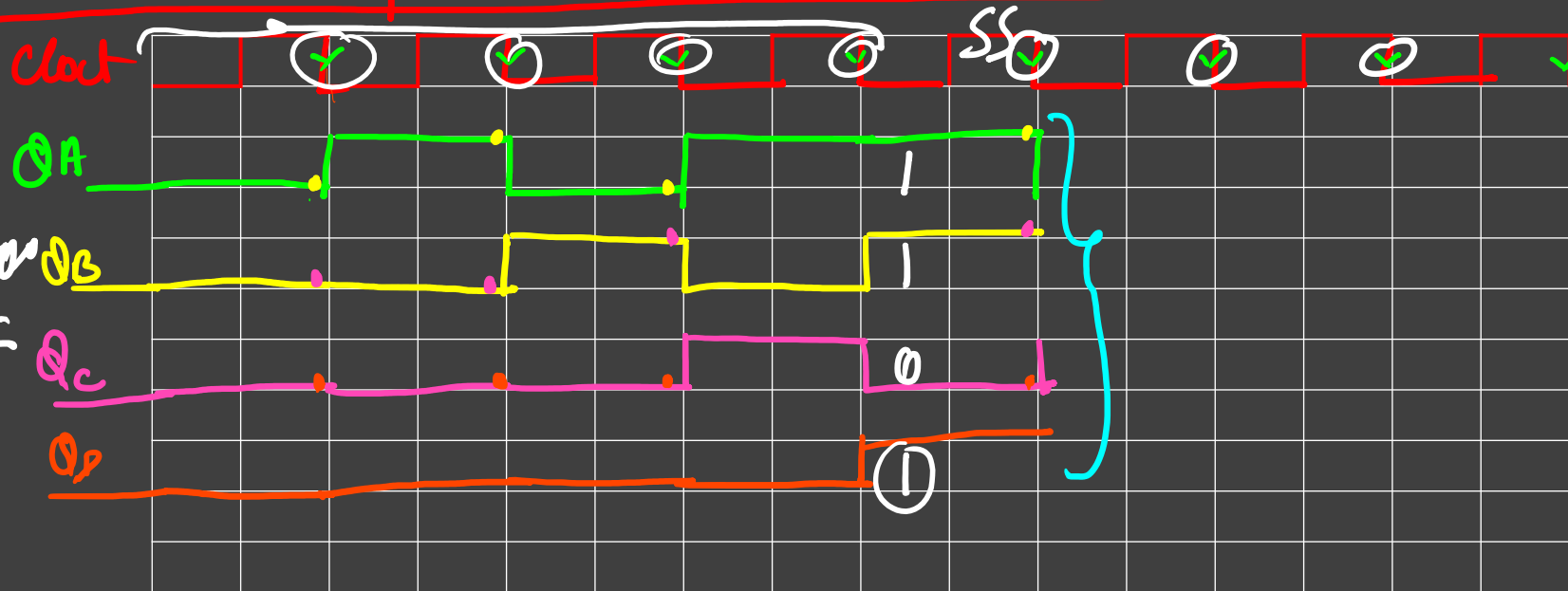
Q How many total no. of clock require to store n bit data in serial mode
A: n clocks



Q How many clock require to read n bit data in parallel mode
A: 2nd clock
No clock

Sequential Logic Circuits Applications

Registers ~~A~~ P/O shift reg.

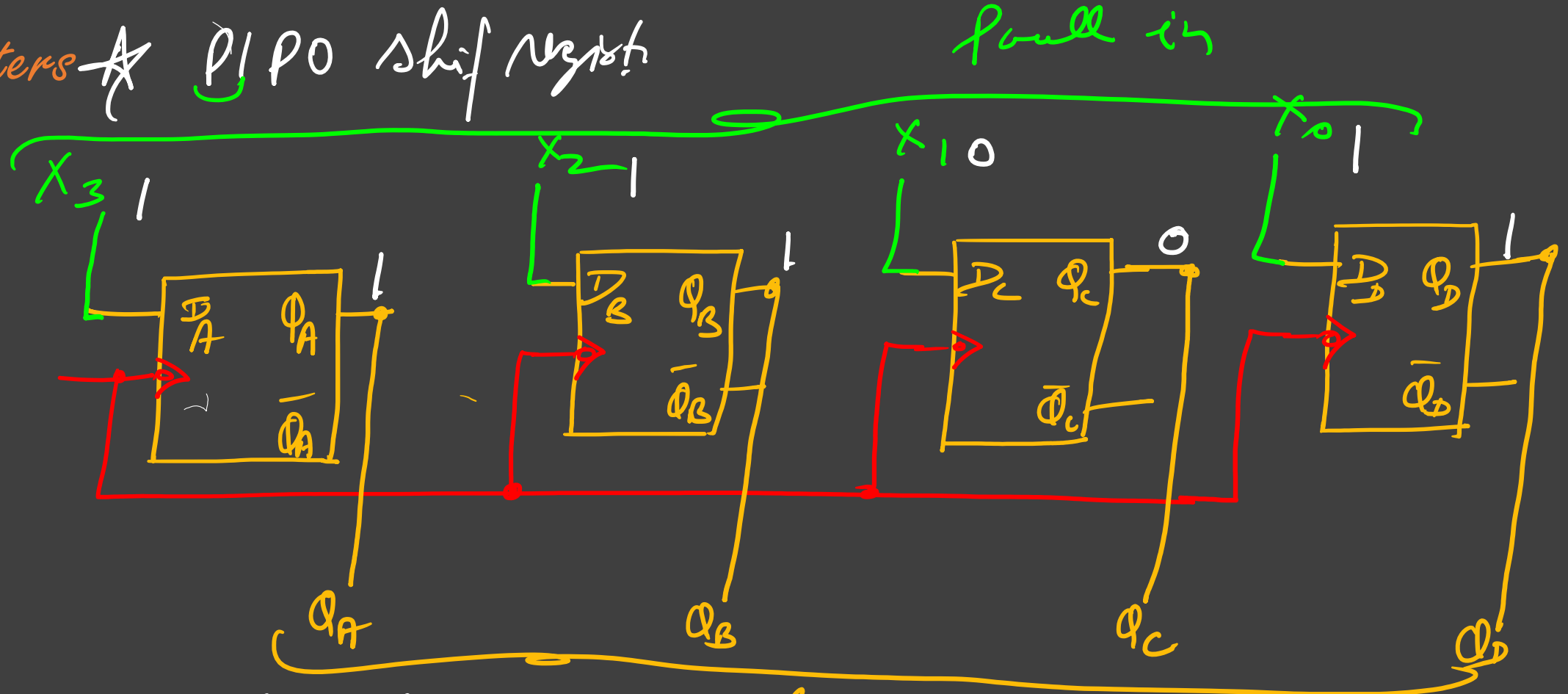


Q: How many clock pulses are required to write the 4-bit data parallel in and out?

A: One clock pulse.

Sequential Logic Circuits Applications

Registers & PISO shift register

4-bit Register

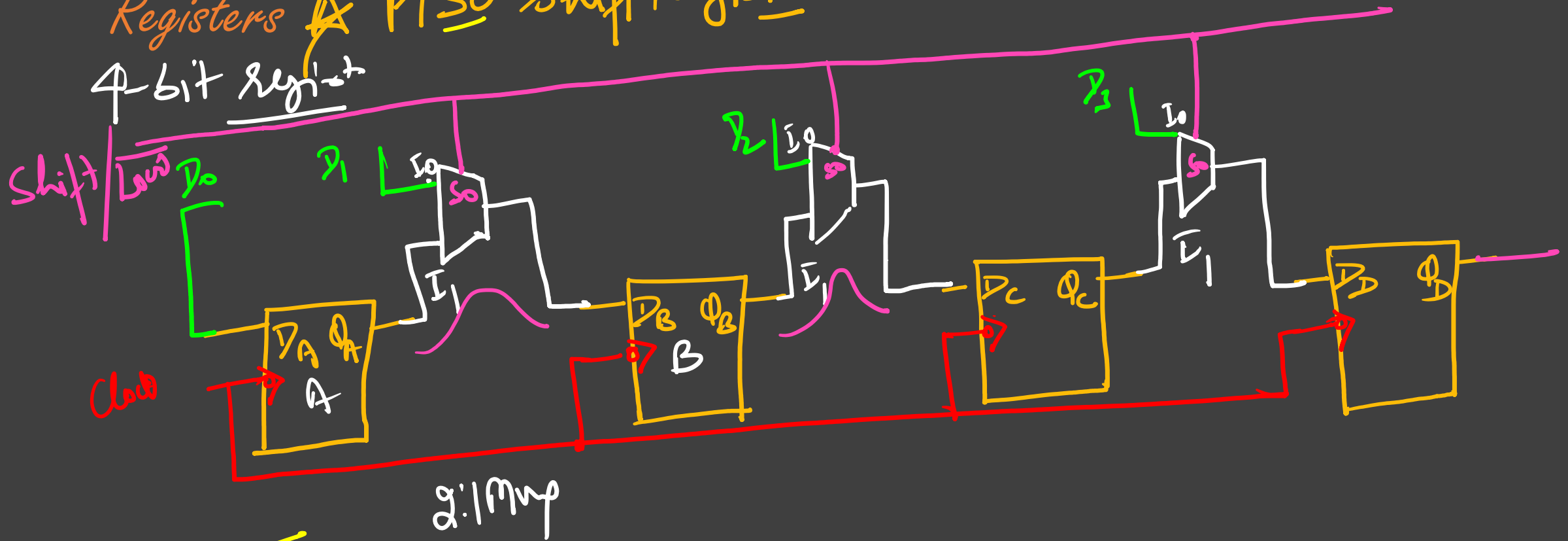

Shift/Load
R/W

Sequential Logic Circuits Applications


Registers

Q: How many Mux required for n -bit PISO shift register?

- A) n
- B) $n+1$
- ☒ C) $n-1$
- D) $2n$

Sequential Logic Circuits Applications

Bidirectional Shift Register

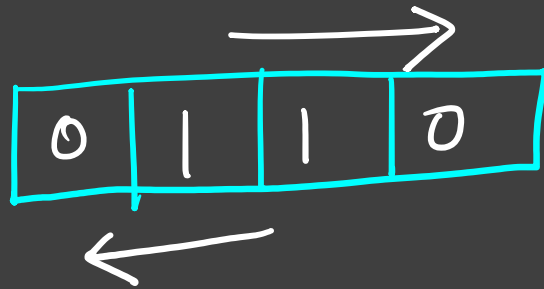

To perform the mult^y & div^y 2.

$$(6)_{10} \xrightarrow{\div 2} (3)_{10}$$

$$(0110)_2 \longleftrightarrow (0011)$$

→ Shift Right
Div


$$(6)_{10} \xrightarrow{\times 2} (12)_{10}$$

$$(0110)_2 \longleftrightarrow (1100)$$

← Shift Left
Multi.

Sequential Logic Circuits Applications

Bidirectional Shift Register

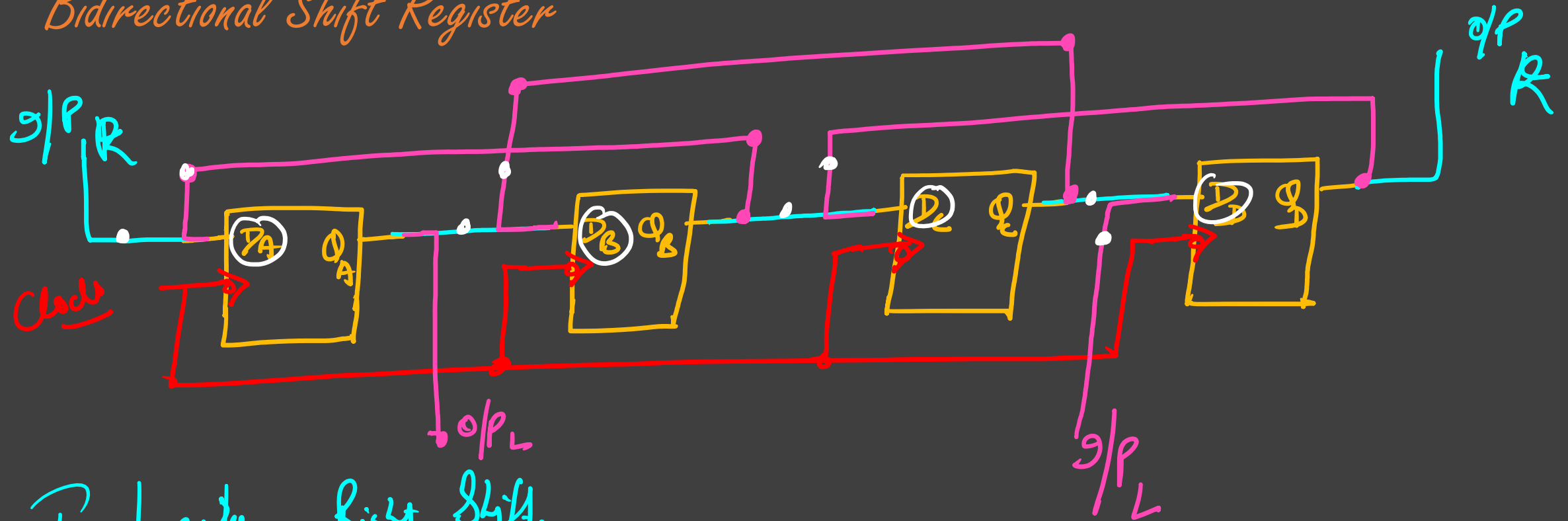

To perform Right Shift.

To perform Left Shift


Bidirectional Shift Register

Sequential Logic Circuits Applications

Bidirectional Shift Register

Q: How many Mux required to make n -bit Bidirectional shift Register

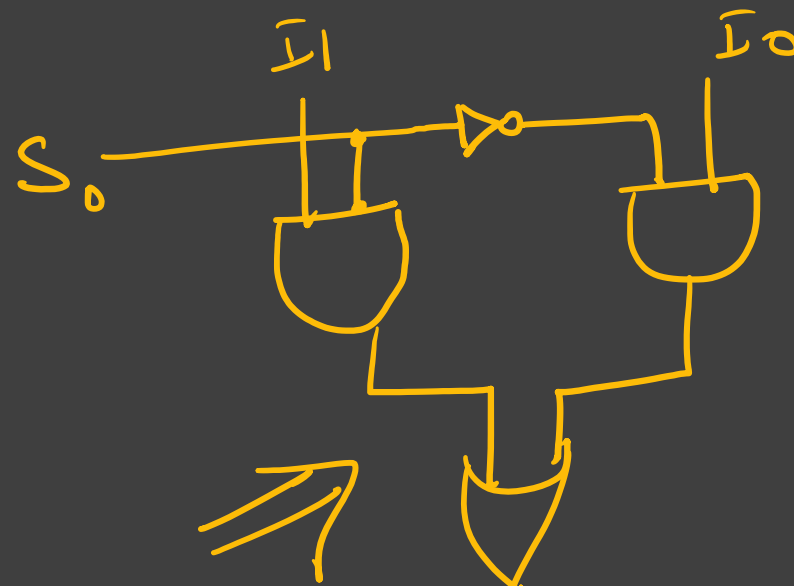- ~~A) n~~
- B) $n-1$
- C) $n+1$
- D) $2n$



$$Y = \overline{S_0} \overline{I_0} + S_0 I_1$$